

# Problem 1.

## Part A

$$V_{b-hi} = 13.8 \text{ KV}$$

$$V_{b-lo} = 2400 \text{ KV}$$

$$S_b = 50 \text{ MVA}$$


$$X_{tr} = 0.08 \text{ p.u.}$$

$$X_{net} = \frac{V_{net}^2}{S_{net-sc}}$$

$$V_{net} = \frac{13.8 \text{ KV}}{V_{b-hi}} = 1.0 \text{ p.u.}$$

$$S_{net-sc} = \frac{300 \text{ MVA}}{S_b} = 6 \text{ p.u.}$$
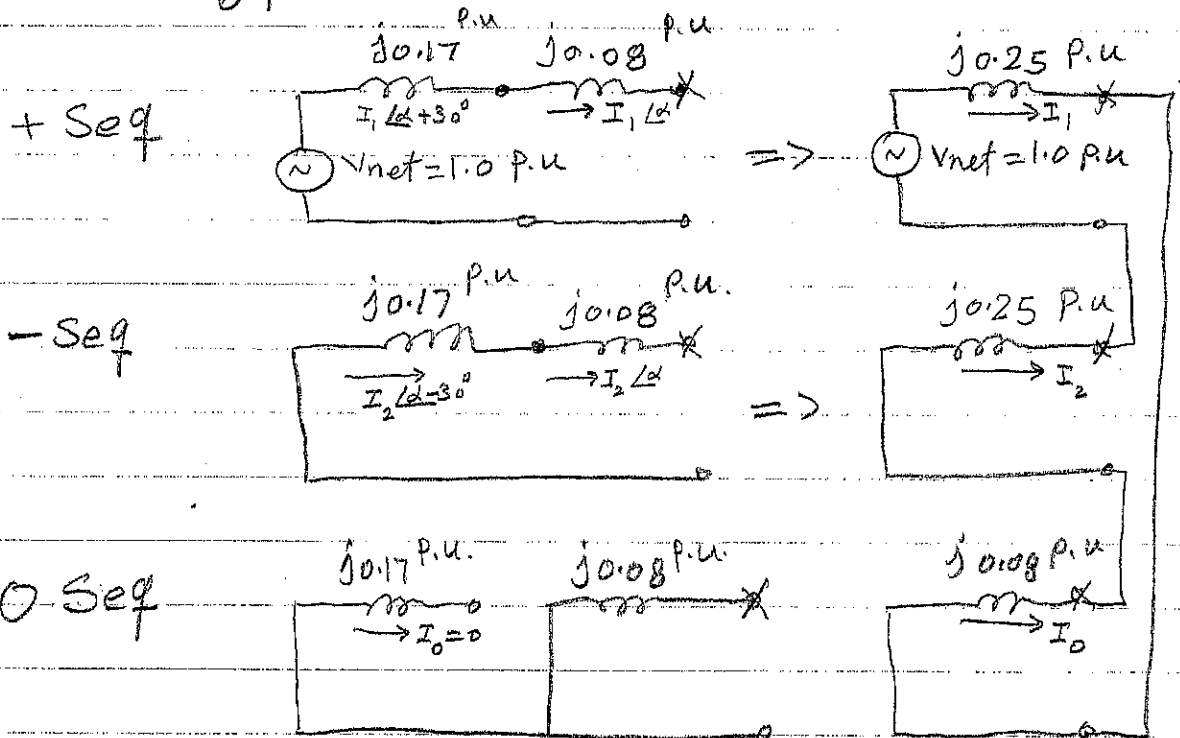
$$X_{net} = \frac{1.0 \text{ p.u.}}{6 \text{ p.u.}} = 0.17 \text{ p.u.}$$



$$\bar{I}_0 = \bar{I}_1 = \bar{I}_2 = \frac{V_{net} = 1.0 \angle 0^\circ}{j0.25 + j0.25 + j0.08} = -j1.74 \text{ p.u.}$$

$$a = 1.0 \angle 120^\circ$$

$$\bar{I}_{abc-LV} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} \bar{I}_0 \\ \bar{I}_1 \\ \bar{I}_2 \end{bmatrix} = \begin{bmatrix} 5.23 \angle -90^\circ \\ 0 \\ 0 \end{bmatrix} \quad \text{Current at LV Side}$$

$$\bar{I}_{abc-nV} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} \bar{I}_0 \\ \bar{I}_1 \angle 30^\circ \\ \bar{I}_2 \angle -30^\circ \end{bmatrix} = \begin{bmatrix} 3.02 \angle -90^\circ \\ 0 \\ 3.02 \angle 90^\circ \end{bmatrix} \text{ p.u.}$$

part B

$$\bar{V}_1 = V_{net} - jX_1 \bar{I}_1 = 0.57 \angle 0^\circ \text{ p.u.}$$

$$\bar{V}_2 = -jX_2 \bar{I}_2 = 0.43 \angle 180^\circ \text{ p.u.}$$

$$\bar{V}_0 = -jX_0 \bar{I}_0 = 0.14 \angle 180^\circ \text{ p.u.}$$

$$\bar{V}_{abc} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} \bar{V}_0 \\ \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = \begin{bmatrix} 0.0 \\ 0.89 \angle -103.59^\circ \\ 0.89 \angle 103.59^\circ \end{bmatrix} \text{ p.u.}$$

## Problem 2.

Use 115 kV Line side as a base.

$$S_b = 100 \text{ MVA}$$

$$V_b = 115 \text{ kV}$$

$$V_{bs} = V_b \frac{13.8 \text{ kV}}{115 \text{ kV}} = 13.8 \text{ kV}$$

$$V_{br} = V_b \frac{24 \text{ kV}}{115 \text{ kV}} = 24 \text{ kV}$$

Generator 1

$$S_{G1} = 200 \text{ MVA}$$

$$X_{G1} = X_{G1}^{\text{old}} \left( \frac{V_{G1}}{V_{bs}} \right)^2 \left( \frac{S_b}{S_{G1}} \right) = 0.1 \left( \frac{13.8 \text{ kV}}{13.8 \text{ kV}} \right)^2 \left( \frac{100 \text{ MVA}}{200 \text{ MVA}} \right) = 0.05 \text{ p.u.}$$

Transformer 1

$$X/R = 25 \quad R = \frac{0.05}{25} = 0.002 \text{ p.u. Can be neglected}$$

$$X_{Tr1} = 0.05 \left( \frac{13.8 \text{ kV}}{13.8 \text{ kV}} \right)^2 \left( \frac{100 \text{ MVA}}{200 \text{ MVA}} \right) = 0.025 \text{ p.u.}$$

Transmission line:

$$X_L = j0.5 \text{ p.u.}$$


$$Y_L = j0.02 \text{ p.u.}$$

transformer 2:

$$X_{Tr2} = 0.1 \left( \frac{24 \text{ kV}}{24 \text{ kV}} \right)^2 \left( \frac{100 \text{ MVA}}{75 \text{ MVA}} \right) = 0.1333 \text{ p.u.}$$

Generator 2:
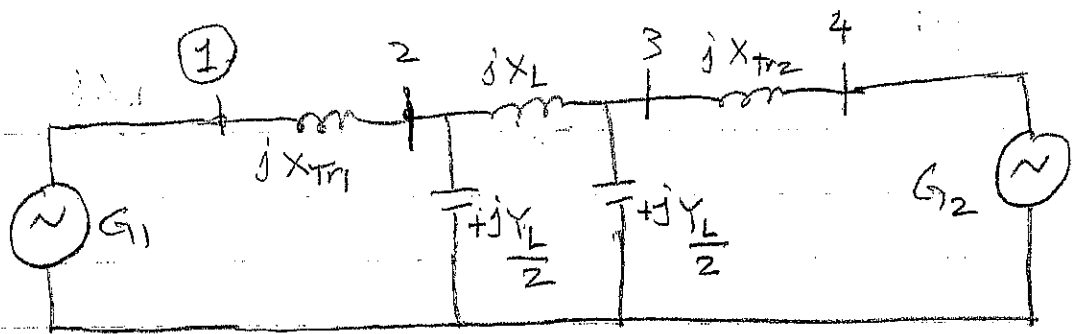
$$X_{G2} = 0.2 \left( \frac{24 \text{ kV}}{24 \text{ kV}} \right)^2 \left( \frac{100 \text{ MVA}}{75 \text{ MVA}} \right) = 0.2667 \text{ p.u.}$$



$$Y_{BUS} = \begin{bmatrix} \frac{1}{jX_{Tr1}} & -\frac{1}{jX_{Tr1}} & 0 & 0 \\ -\frac{1}{jX_{Tr1}} & \left( \frac{1}{jX_{Tr1}} + \frac{1}{jX_L} + j\frac{Y_L}{2} \right) & -\frac{1}{jX_L} & 0 \\ 0 & -\frac{1}{jX_L} & \left( \frac{1}{jX_L} + \frac{1}{jX_{Tr2}} + j\frac{Y_L}{2} \right) & -\frac{1}{jX_{Tr2}} \\ 0 & 0 & -\frac{1}{jX_{Tr2}} & \frac{1}{jX_{Tr2}} \end{bmatrix}$$

$$Y_{BUS} = \begin{bmatrix} -j40 & j40 & 0 & 0 \\ j40 & -j41.99 & j2 & 0 \\ 0 & j2 & -j9.49 & j7.5 \\ 0 & 0 & j7.5 & -j7.5 \end{bmatrix}$$

# problem 3: Method one

Part A

$$Z_{tot} = j0.45 + j0.35 + j0.34 + j0.9 = j2.04$$

$$I = \frac{1.0 \angle 0}{Z_{tot}} = 0.4902 \angle -90^\circ$$


$$V_{load} = I \cdot Z_{load} = 0.4902 \angle -90^\circ \cdot 0.9 \angle 90^\circ$$

$$V_{load} = 0.441 \text{ p.u.}$$


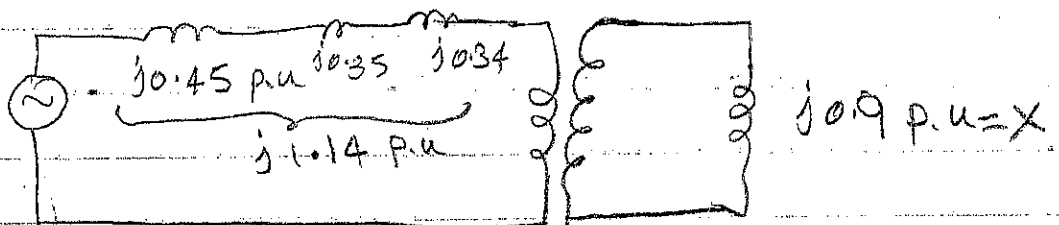
Part B



$$n = \frac{1}{10} \quad n' = \frac{1}{8}$$

$$a = \frac{n'}{n} = \frac{\frac{1}{8}}{\frac{1}{10}} = 1.25$$



$$Y = 0.877$$

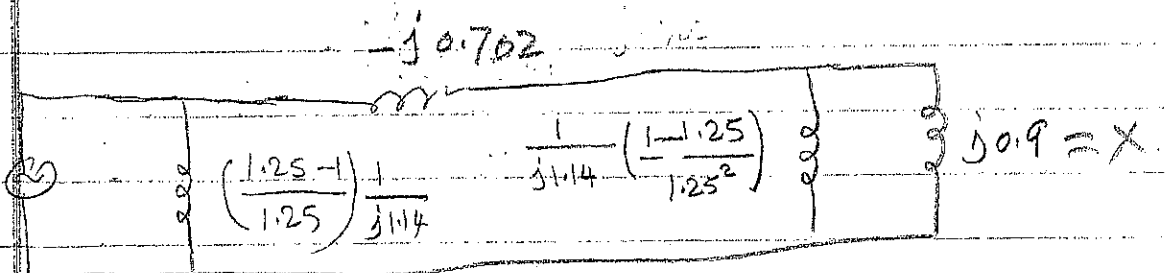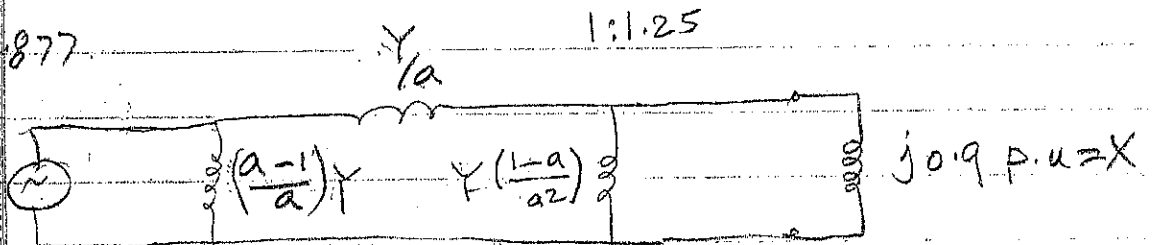

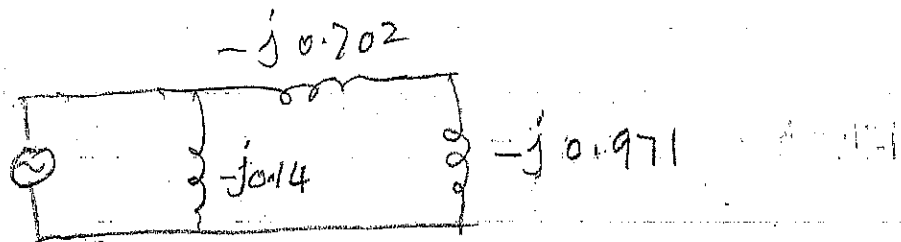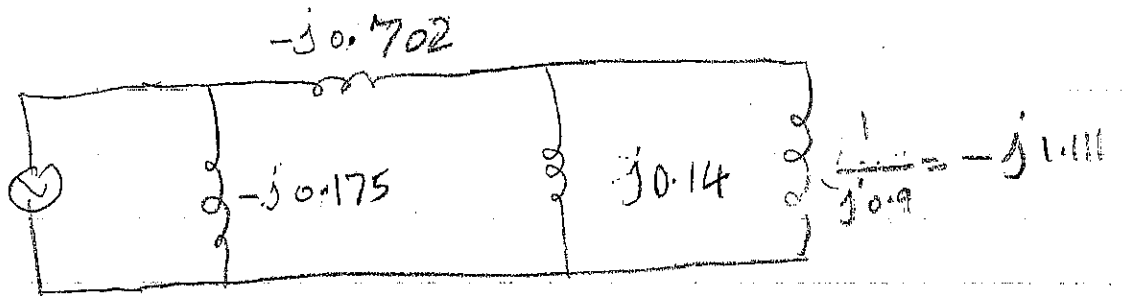

$$V_2 = \frac{1}{-j0.971} \cdot \frac{1.0 \angle 0}{\frac{1}{-j0.702} + \frac{1}{-j0.971}}$$

$$V_2 = j1.03 \cdot \frac{1.0 \angle 0}{j1.425 + j1.03} = 0.42 \text{ p.u.}$$

### Problem 3: Method two

Part A:

$$Z_{total} = j0.45 + j0.35 + j0.34 + j0.9 = j2.04$$

$$I = \frac{1.0 \angle 0^\circ}{Z_{total}} = 0.4902 \angle -90^\circ$$


$$V_{load} = I \cdot Z_{Load} = 0.4902 \angle -90^\circ \times 0.9 \angle 90^\circ$$

$$V_{load} = 0.441 \text{ p.u.}$$

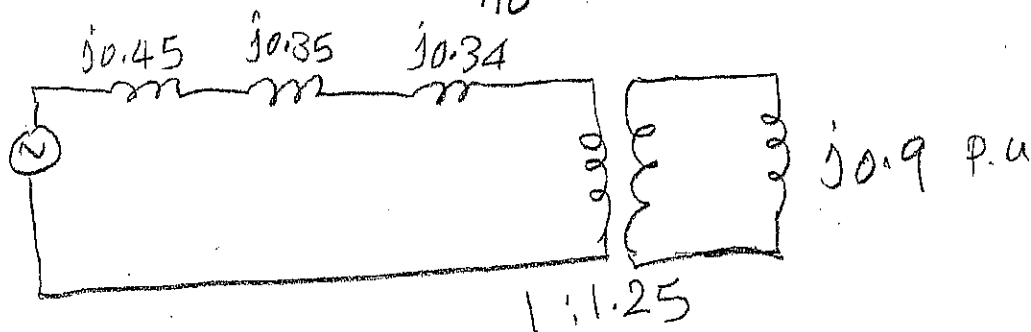Part B

$$n = \frac{1}{10} \quad n' = \frac{1}{8}$$

$$a = \frac{n'}{n} = \frac{\frac{1}{8}}{\frac{1}{10}} = 1.25$$



$$Z_{\text{Load-p}} = j0.9 \left( \frac{1}{1.25} \right)^2 = j0.576$$

$$I_p = \frac{1.0 \angle 0^\circ}{j0.45 + j0.35 + j0.34 + j0.576}$$

$$I_p = -j0.583 = 0.583 \angle -90^\circ$$

$$I_s = I_p \left( \frac{1}{1.25} \right) = 0.583 \angle -90^\circ \times \frac{1}{1.25}$$

$$I_s = 0.466 \angle -90^\circ$$

$$V_{\text{Load}} = j0.9 \times 0.466 \angle -90^\circ$$

$$V_{\text{Load}} = 0.42 \text{ p.u.}$$