

## Solving for multiply unknowns using Kirchoff's Rules

Rule 1:	$I_1 + I_2 - I_3 = 0$
Rule 2:	$I_1 R_1 + I_3 R_3 = V_1$ (loop 1)
	$I_2 R_2 + I_3 R_3 = V_2$ (loop 2)

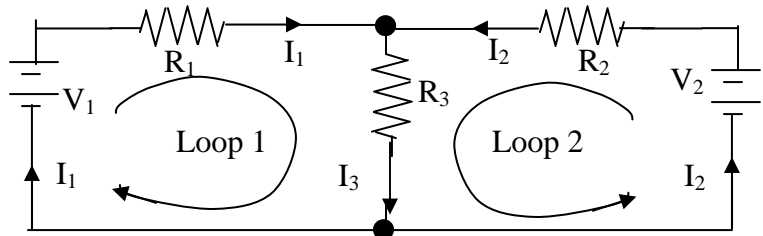


Figure 18-3

### Method 1 Algebraically

Given  $R_1, R_2, R_3, V_1$  and  $V_2$

From Rule 1 we have  $I_3 = I_1 + I_2$ . Substitute this in for  $I_3$  in rule 2 Loops 1 and 2.

We have

Grouping the unknown variables

**Loop1**  $I_1 R_1 + (I_1 + I_2) R_3 = V_1$  and

$(R_1 + R_3) I_1 + R_3 I_2 = V_1$  [ 1 ]

**Loop2**  $I_2 R_2 + (I_1 + I_2) R_3 = V_2$  and

$I_1 R_3 + I_2 (R_2 + R_3) = V_2$  [ 2 ]

To find  $I_1$  you must first eliminate  $I_2$

Multiply [1] by  $(R_2 + R_3)$        $(R_2 + R_3)(R_1 + R_3) I_1 + (R_2 + R_3) R_3 I_2 = V_1(R_2 + R_3)$

Multiply [2] by  $-R_3$        $-I_1(R_3)^2 - R_3(R_2 + R_3) I_2 = -V_2 R_3$

Add the two equations       $I_1((R_2 + R_3)(R_1 + R_3) - (R_3)^2) + 0 = V_1(R_2 + R_3) - V_2 R_3$

Solve for  $I_1$

$$I_1 = \frac{V_1(R_2 + R_3) - V_2 R_3}{(R_2 + R_3)(R_1 + R_3) - (R_3)^2}$$

To find  $I_2$  you must first eliminate  $I_1$

Multiply [1] by  $-R_3$        $-R_3(R_1 + R_3) I_1 - (R_3)^2 I_2 = -V_1 R_3$

Multiply [2] by  $(R_1 + R_3)$        $(R_3)(R_1 + R_3) I_1 + (R_2 + R_3)(R_1 + R_3) I_2 = V_2(R_1 + R_3)$

Add the two equations       $0 + I_2((R_2 + R_3)(R_1 + R_3) - (R_3)^2) = V_2(R_1 + R_3) - V_1 R_3$

Solve for  $I_2$

$$I_2 = \frac{V_2(R_1 + R_3) - V_1 R_3}{(R_2 + R_3)(R_1 + R_3) - (R_3)^2}$$

### Method 2 Matrices

If your calculator is capable of creating matrices generate a 3 x 3 matrix for A

Where we will be solving for the unknown currents set the unknown currents to 1

$$A = \begin{bmatrix} 1 & 1 & -1 \\ R_1 & 0 & R_3 \\ 0 & R_2 & R_3 \end{bmatrix} \begin{array}{l} \text{Rule 1} \\ \text{Loop 1} \\ \text{Loop} \end{array} \quad \text{Also a 3 x 1 matrix } B = \begin{bmatrix} 0 \\ V_1 \\ V_2 \end{bmatrix}$$

Then  $A^{-1} B$  yields the three unknown currents and yield

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$