

# PHYS 1444 – Section 001

## Lecture #21

*Dr. Koymen*

- AC Circuit w/ Resistance only
- AC Circuit w/ Inductance only
- AC Circuit w/ Capacitance only
- AC Circuit w/ LRC



# Why do we care about circuits on AC?

- The circuits we've learned so far contain resistors, capacitors and inductors and have been connected to a DC source or a fully charged capacitor
  - What? This does not make sense.
  - The inductor does not work as an impedance unless the current is changing. So an inductor in a circuit with DC source does not make sense.
  - Well, actually it does. When does it impede the current flow?
    - Immediately after the circuit is connected to the source so the current is still changing.
    - So what?
      - It causes the change of magnetic flux.
  - Now does it make sense?
- Anyhow, learning the responses of resistors, capacitors and inductors in a circuit connected to an AC emf source is important. Why is this?
  - Since most the generators produce sinusoidal current
  - Any voltage that varies over time can be expressed in the superposition of sine and cosine functions



# AC Circuits – the preamble

- Do you remember how the rms and peak values for current and voltage are related?

$$V_{rms} = \frac{V_0}{\sqrt{2}} \quad I_{rms} = \frac{I_0}{\sqrt{2}}$$

- The symbol for an AC power source is



- We assume that the voltage gives rise to current


$$I = I_0 \sin 2\pi ft = I_0 \sin \omega t$$

– where  $\omega = 2\pi f$


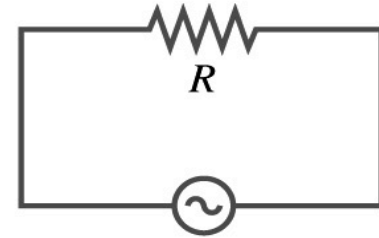
# AC Circuit w/ Resistance only

- What do you think will happen when an ac source is connected to a resistor?
- From Kirchhoff's loop rule, we obtain



$$V - IR = 0$$


- Thus

$$V = I_0 R \sin \omega t = V_0 \sin \omega t$$

– where  $V_0 = I_0 R$

- What does this mean?

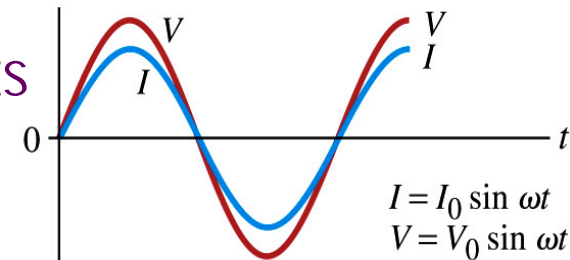- Current is 0 when voltage is 0 and current is in its peak when voltage is in its peak.
- Current and voltage are “in phase”



- Energy is lost via the transformation into heat at an average rate

$$\bar{P} = \bar{I} \bar{V} = I_{rms}^2 R = V_{rms}^2 / R$$



# AC Circuit w/ Inductance only

- From Kirchhoff's loop rule, we obtain

$$V - L \frac{dI}{dt} = 0$$

- Thus



$$V = L \frac{dI}{dt} = L \frac{d(I_0 \sin \omega t)}{dt} = \omega L I_0 \cos \omega t$$

- Using the identity  $\cos \theta = \sin(\theta + 90^\circ)$
- $V = \omega L I_0 \sin(\omega t + 90^\circ) = V_0 \sin(\omega t + 90^\circ)$ 
  - where  $V_0 = \omega L I_0$
- What does this mean?

- Current and voltage are "out of phase by  $\pi/2$  or  $90^\circ$ ".
- In other words the current reaches its peak  $\frac{1}{4}$  cycle after the voltage

- What happens to the energy?

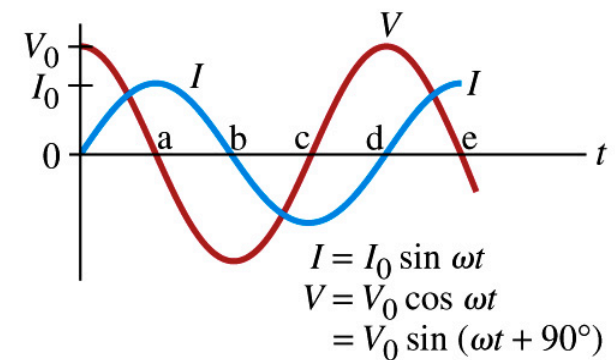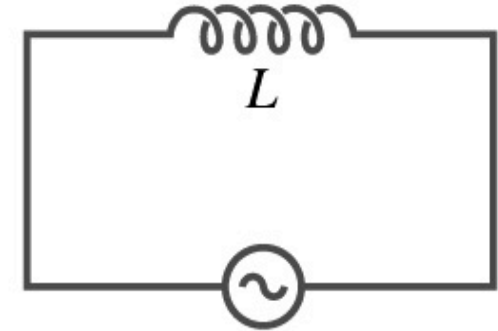- No energy is dissipated
- The average power is 0 at all times
- The energy is stored temporarily in the magnetic field
- Then released back to the source



# AC Circuit w/ Inductance only

- How are the resistor and inductor different in terms of energy?
  - Inductor Stores the energy temporarily in the magnetic field and then releases it back to the emf source
  - Resistor Does not store energy but transforms it to thermal energy, getting it lost to the environment
- How are they the same?
  - They both impede the flow of charge
  - For a resistance  $R$ , the peak voltage and current are related to  $V_0 = I_0 R$
  - Similarly, for an inductor we can write  $V_0 = I_0 X_L$ 
    - Where  $X_L$  is the inductive reactance of the inductor  $X_L = \omega L$  0 when  $\omega=0$ .
    - What do you think is the unit of the reactance?  $\Omega$
    - The relationship  $V_0 = I_0 X_L$  is not valid at a particular instance. Why not?
      - Since  $V_0$  and  $I_0$  do not occur at the same time



$$V_{rms} = I_{rms} X_L$$

is valid!

# Example 30 – 9

**Reactance of a coil.** A coil has a resistance  $R=1.00\Omega$  and an inductance of  $0.300\text{H}$ . Determine the current in the coil if (a)  $120\text{ V dc}$  is applied to it; (b)  $120\text{ V ac (rms)}$  at  $60.0\text{Hz}$  is applied.

Is there a reactance for dc? Nope. Why not? Since  $\omega=0$ ,  $X_L = \omega L = 0$

So for dc power, the current is from Kirchhoff's rule  $V - IR = 0$

$$I_0 = \frac{V_0}{R} = \frac{120\text{V}}{1.00\Omega} = 120\text{A}$$

For an ac power with  $f=60\text{Hz}$ , the reactance is

$$X_L = \omega L = 2\pi fL = 2\pi \cdot (60.0\text{s}^{-1}) \cdot 0.300\text{H} = 113\Omega$$


Since the resistance can be ignored compared to the reactance, the rms current is

$$I_{rms} \approx \frac{V_{rms}}{X_L} = \frac{120\text{V}}{113\Omega} = 1.06\text{A}$$


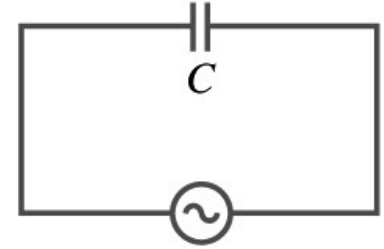
# AC Circuit w/ Capacitance only

- What happens when a capacitor is connected to a dc power source?



- The capacitor quickly charges up.
  - There is no steady current flow in the circuit
    - Since a capacitor prevents the flow of a dc current
- What do you think will happen if it is connected to an ac power source?
    - The current flows continuously. Why?
    - When the ac power turns on, charge begins to flow one direction, charging up the plates
    - When the direction of the power reverses, the charge flows in the opposite direction



# AC Circuit w/ Capacitance only

- From Kirchoff's loop rule, we obtain

$$V = \frac{Q}{C}$$

- Current at any instance is  $I = \frac{dQ}{dt} = I_0 \sin \omega t$

- Thus, the charge Q on the plate at any instance is

$$Q = \int_{Q=0}^Q dQ = \int_{t=0}^t I_0 \sin \omega t dt = -\frac{I_0}{\omega} \cos \omega t$$

- The voltage across the capacitor is


$$V = \frac{Q}{C} = -I_0 \frac{1}{\omega C} \cos \omega t$$

- Using the identity  $\cos \theta = -\sin(\theta - 90^\circ)$

$$V = I_0 \frac{1}{\omega C} \sin(\omega t - 90^\circ) = V_0 \sin(\omega t - 90^\circ)$$

- Where

- $V_0 = \frac{I_0}{\omega C}$

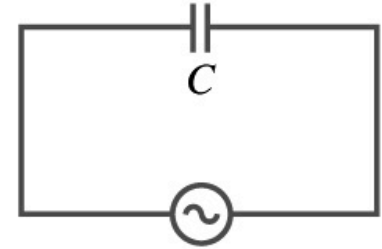


# AC Circuit w/ Capacitance only

- So the voltage is  $V = V_0 \sin(\omega t - 90^\circ)$
- What does this mean?
  - Current and voltage are “out of phase by  $\pi/2$  or  $90^\circ$ ” but in this case, the voltage reaches its peak  $\frac{1}{4}$  cycle after the current

- What happens to the energy?

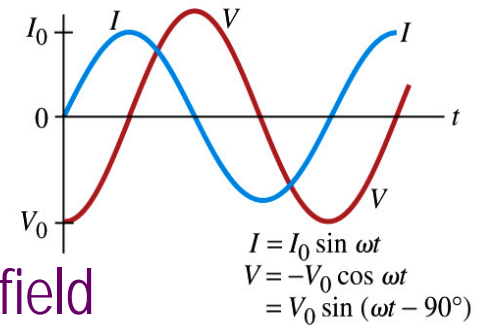- No energy is dissipated
- The average power is 0 at all times
- The energy is stored temporarily in the electric field
- Then released back to the source



- Relationship between the peak voltage and the peak current in the capacitor can be written as  $V_0 = I_0 X_C$

- Where the capacitance reactance  $X_C$  is defined as
- Again, this relationship is only valid for rms quantities

$$X_C = \frac{1}{\omega C}$$


Infinite when  $\omega=0$ .

$$V_{rms} = I_{rms} X_C$$


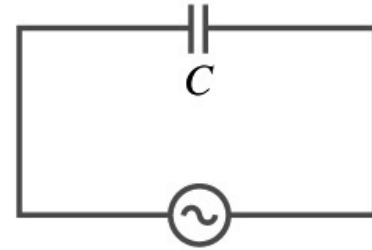
# Example 30 – 10

Capacitor reactance. What are the peak and rms current in the circuit in the figure if  $C=1.0\mu\text{F}$  and  $V_{\text{rms}}=120\text{V}$ ? Calculate for (a)  $f=60\text{Hz}$ , and then for (b)  $f=6.0\times 10^5\text{Hz}$ .



The peak voltage is  $V_0 = \sqrt{2}V_{\text{rms}} = 120\text{V} \cdot \sqrt{2} = 170\text{V}$

The capacitance reactance is

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} = \frac{1}{2\pi \cdot (60\text{s}^{-1}) \cdot 1.0 \times 10^{-6}\text{F}} = 2.7\text{k}\Omega$$

Thus the peak current is

$$I_0 = \frac{V_0}{X_C} = \frac{170\text{V}}{2.7\text{k}\Omega} = 63\text{mA}$$

The rms current is

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{X_C} = \frac{120\text{V}}{2.7\text{k}\Omega} = 44\text{mA}$$



# AC Circuit w/ LRC

- The voltage across each element is

- $V_R$  is in phase with the current
- $V_L$  leads the current by  $90^\circ$
- $V_C$  lags the current by  $90^\circ$

- From Kirchhoff's loop rule


- $V = V_R + V_L + V_C$

- However since they do not reach the peak voltage at the same time, the peak voltage of the source  $V_0$  will not equal

$$V_{R0} + V_{L0} + V_{C0}$$


- The rms voltage also will not be the simple sum of the three

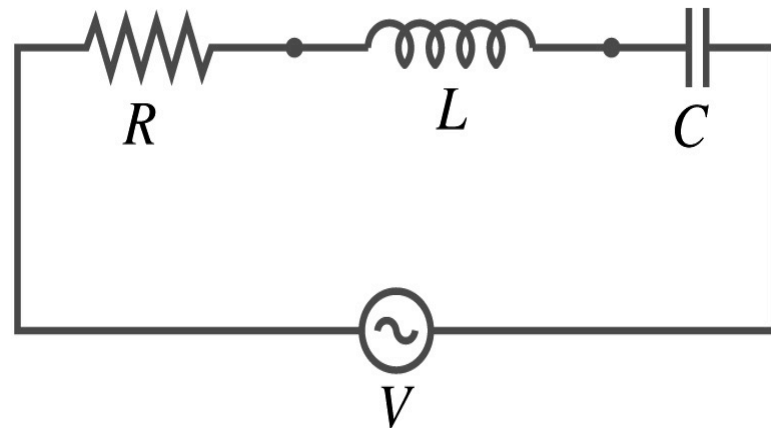- Let's try to find the total impedance, peak current  $I_0$  and the phase difference between  $I_0$  and  $V_0$ .


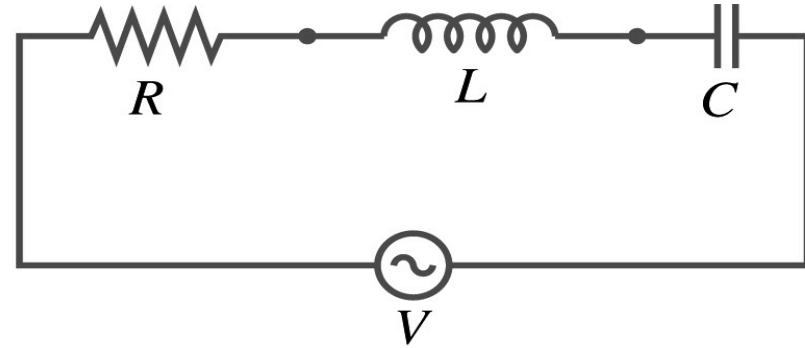
# AC Circuit w/ LRC

- The current at any instance is the same at all point in the circuit
  - The currents in each elements are in phase
  - Why?
    - Since the elements are in series
  - How about the voltage?
    - They are not in phase.



- The current at any given time is



$$I = I_0 \sin \omega t$$

- The analysis of LRC circuit is done using the “phasor” diagram in which arrows are drawn in an xy plane to represent the amplitude of each voltage, just like vectors
  - The lengths of the arrows represent the magnitudes of the peak voltages across each element;  $V_{R0} = I_0 R$ ,  $V_{L0} = I_0 X_L$  and  $V_{C0} = I_0 X_C$
  - The angle of each arrow represents the phase of each voltage relative to the current, and the arrows rotate at the angular frequency  $\omega$  to take into account the time dependence.
    - The projection of each arrow on y axis represents voltage across each element at any given time


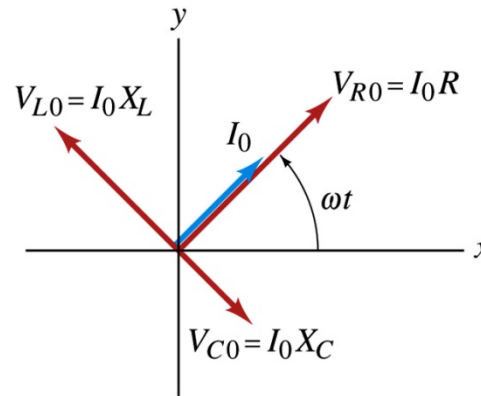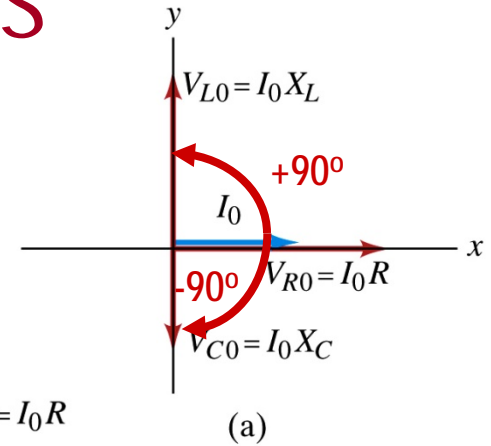
# Phasor Diagrams

- At  $t=0$ ,  $I=0$ .
  - Thus  $V_{R0}=0$ ,  $V_{L0}=I_0X_L$ ,  $V_{C0}=I_0X_C$
- At  $t=t$ ,  $I = I_0 \sin \omega t$




- Thus, the voltages (y-projections) are

$$V_R = V_{R0} \sin \omega t$$


$$V_L = V_{L0} \sin (\omega t + 90^\circ)$$
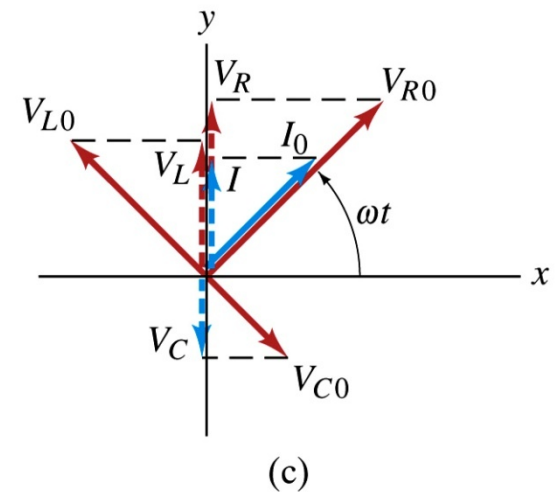
$$V_C = V_{C0} \sin (\omega t - 90^\circ)$$


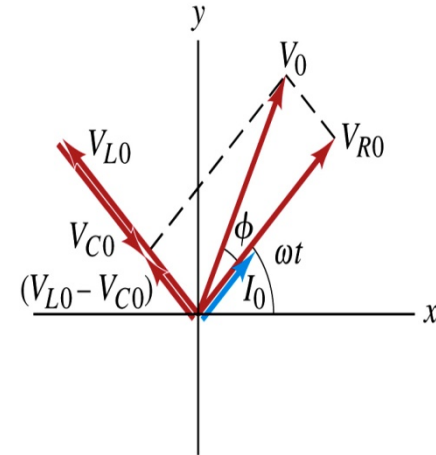
# AC Circuit w/ LRC

- Since the sum of the projections of the three vectors on the y axis is equal to the projection of their sum,
  - The sum of the projections represents the instantaneous voltage across the whole circuit which is the source voltage
  - So we can use the sum of all vectors as the representation of the peak source voltage  $V_0$ .



- $V_0$  forms an angle  $\phi$  to  $V_{R0}$  and rotates together with the other vectors as a function of time,  $V = V_0 \sin(\omega t + \phi)$
- We determine the total impedance  $Z$  of the circuit defined by the relationship  $V_{rms} = I_{rms} Z$  or  $V_0 = I_0 Z$
- From Pythagorean theorem, we obtain

$$V_0 = \sqrt{V_{R0}^2 + (V_{L0} - V_{C0})^2} = \sqrt{I_0^2 R^2 + I_0^2 (X_L - X_C)^2} = I_0 \sqrt{R^2 + (X_L - X_C)^2} = I_0 Z$$

- Thus the total impedance is  $Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$



# AC Circuit w/ LRC

- The phase angle  $\phi$  is

$$\tan \phi = \frac{V_{L0} - V_{C0}}{V_{R0}} = \frac{I_0 (X_L - X_C)}{I_0 R} = \frac{(X_L - X_C)}{R}$$

- or

$$\cos \phi = \frac{V_{R0}}{V_0} = \frac{I_0 R}{I_0 Z} = \frac{R}{Z}$$

- What is the power dissipated in the circuit?

- Which element dissipates the power?
- Only the resistor

- The average power is  $\bar{P} = I_{rms}^2 R$

- Since  $R = Z \cos \phi$

- We obtain  $\bar{P} = I_{rms}^2 Z \cos \phi = I_{rms} V_{rms} \cos \phi$

- The factor  $\cos \phi$  is referred as the power factor of the circuit

- For a pure resistor,  $\cos \phi = 1$  and  $\bar{P} = I_{rms} V_{rms}$

- For a capacitor or inductor alone  $\phi = -90^\circ$  or  $+90^\circ$ , so  $\cos \phi = 0$  and  $\bar{P} = 0$ .

