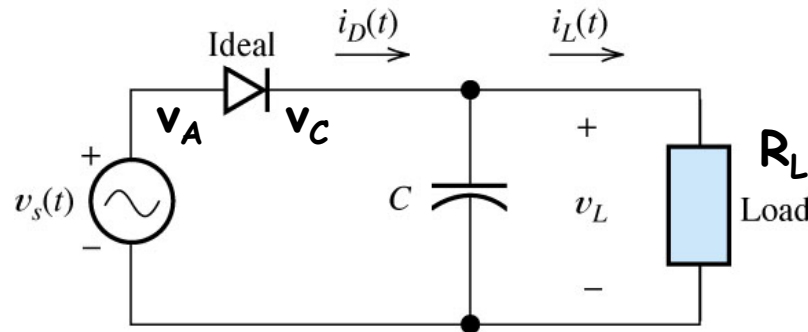


Lecture 09
EE 2303/001-Electronics I
February 18, 2009

Professor Ronald L. Carter
ronc@uta.edu
<http://www.uta.edu/ronc/>

Half-wave rectifier




(a) Circuit diagram

Figure 3.12a Half-wave rectifier with smoothing capacitor.

- Maximum reverse bias on diode?
 - If $R_L C \gg T$, then $v_C = +V_m$ for all time
 - In negative half-cycle, $v_A \geq -V_m$
 - Thus the maximum reverse bias is
$$(v_C - v_A)_{\max} = 2V_m$$
 - For $C = 0$, $(v_C - v_A)_{\max} = V_m$ because $i_L R_L = 0$ in the negative half-cycle


Full-wave rectifier

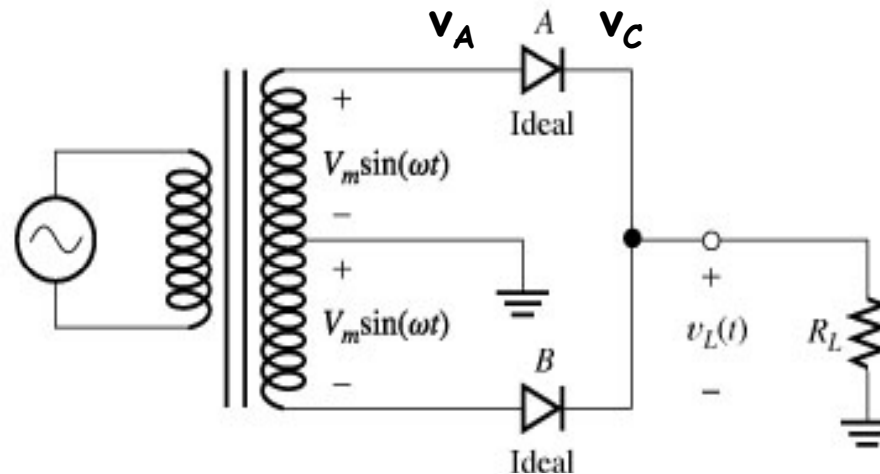

(a) Circuit diagram

Figure 3.13 Full-wave rectifier.

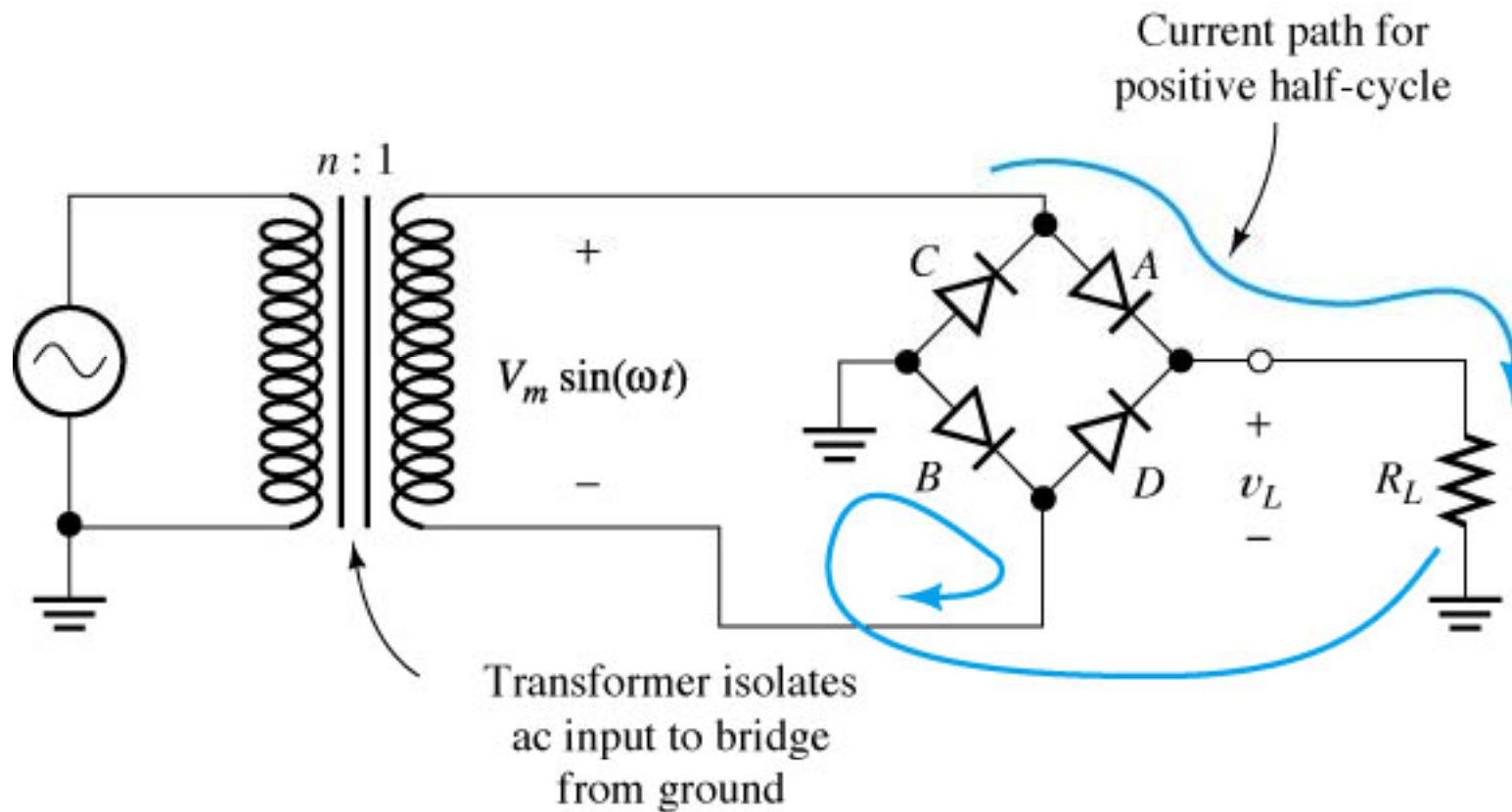- Effect on V_{rmax} ?
 - If filter capacitor is used, the same argument as half-wave rectifier may be used, for the positive half-cycle.
 - For $C=0$, and since $v_L(t)$ always peaks at $+V_m$, then $(v_C - v_A)_{max} = 2 V_m$ for each diode.




- Effect on V_{rmax} ?
 - With and without C the maximum reverse bias is V_m .

SILICON ZENER DIODES

1N746 to 1N759
DO-35 400mW

DO-35 Glass Axial Package

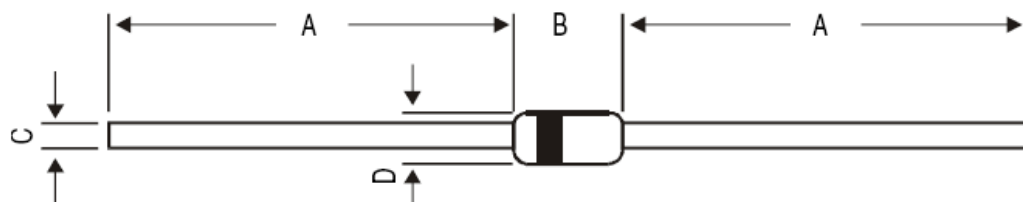

DIM	MIN	MAX
A	25.40	—
B	3.03	4.44
C	0.46	0.56
D	1.52	2.29

- NOTES
 1. Cathode is marked by Band.
 2. All dimensions are in mm.

Hermetically Sealed Glass Package Zener Diodes

ABSOLUTE MAXIMUM RATINGS

DESCRIPTION	SYMBOL	VALUE	UNIT
Zener Voltage	ZV	3.3 to 12	V
D C Power Dissipation	PD	400	mW
Derating Above 50 deg C		3.2	mW/deg C
Operating & Storage Junction Temperature Range	Tj, Tstg	-65 to +175	deg C

ELECTRICAL CHARACTERISTICS (Ta=25 deg C Unless otherwise Specified, VF < 1.5V @ 200mA)

Device Type# (1)	Nominal* Zener Voltage VZ @ IZT (V)	Zener Test Current IZT (mA)	Maximum Zener Impedance Zzt @ IZT (Ohms)	Maximum Reverse Current @ 25 deg C max (uA)	Maximum Reverse Current @ +150 deg C max (uA)	VR (V)	Maximum Zener Current IZM (mA)	Typ Temp Coeff of Zener Voltage *vz (% deg C)
1N750	4.7	20	19	2.0	30	1.0	75	-0.015

http://www.datasheetpro.com/316313_download_1N750_datasheet.html

Diode Equations for DC Current [1]

$$I_d = \text{area} \cdot (I_{fwd} - I_{rev})$$

$$I_{fwd} = \text{forward current} = I_{nrm} \cdot K_{inj} + I_{rec} \cdot K_{gen}$$

$$I_{nrm} = \text{normal current} = I_S \cdot (e^{V_d / (N \cdot V_t)} - 1)$$

$$\text{if: } IKF > 0$$

then:

$$K_{inj} = \text{high-injection factor} = (IKF / (IKF + I_{nrm}))^{1/2}$$

$$\text{else: } K_{inj} = 1$$

$$I_{rec} = \text{recombination current} = I_{SR} \cdot (e^{V_d / (N_R \cdot V_t)} - 1)$$

$$K_{gen} = \text{generation factor} = ((1 - V_d / V_J)^2 + 0.005) M / 2$$

$$I_{rev} = \text{reverse current} = I_{revhigh} + I_{revlow}$$

$$I_{revhigh} = I_{BV} \cdot \exp\{-(V_d + BV) / (N_{BV} \cdot V_t)\}$$

$$I_{revlow} = I_{BVL} \cdot \exp\{-(V_d + BV) / (N_{BVL} \cdot V_t)\}$$


.model D1N750-X D(
Is=880.5E-18
Rs=.25
Ikf=0
N=1
Xti=3
Eg=1.11
Cjo=175p
M=.5516
Vj=.75
Fc=.5
Isr=1.859n
Nr=2

L09, Feb 18

Bv=4.7
Ibv=20.245m
Nbv=1.6989
Ibvl=1.9556m
Nbv1=14.976
Tbv1=-21.277u)
*Motorola pid=1N750
case=DO-35
* 89-9-18 gjg
* Vz = 4.7 @ 20mA, Zz =
300 @ 1mA, Zz = 12.5
@ 5mA, Zz = 2.6 @
20mA

*\$


(A) ZenerCircuit.dat

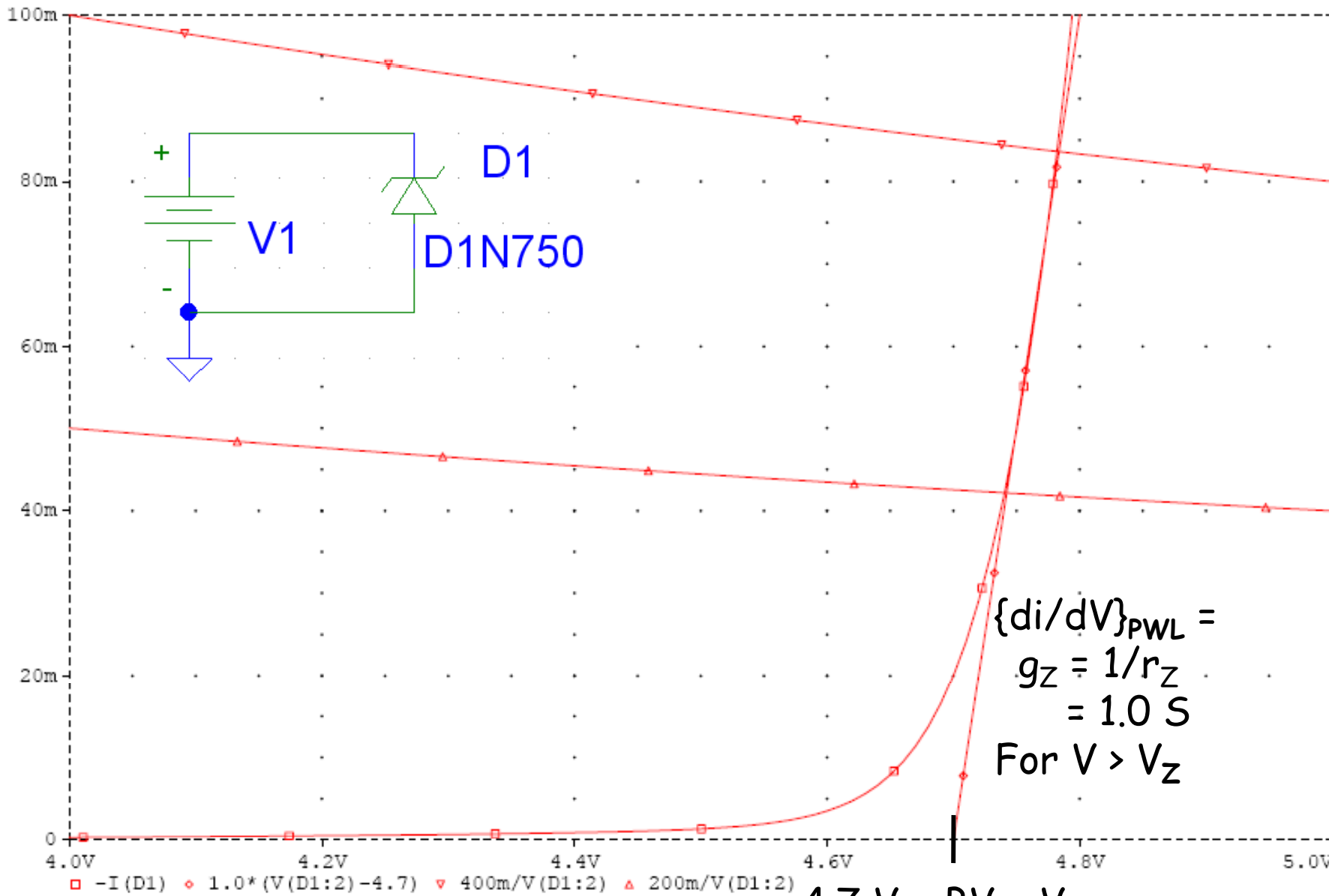

L09, Feb 18

4.7 V = BV = V_Z

(A) ZenerChar.dat

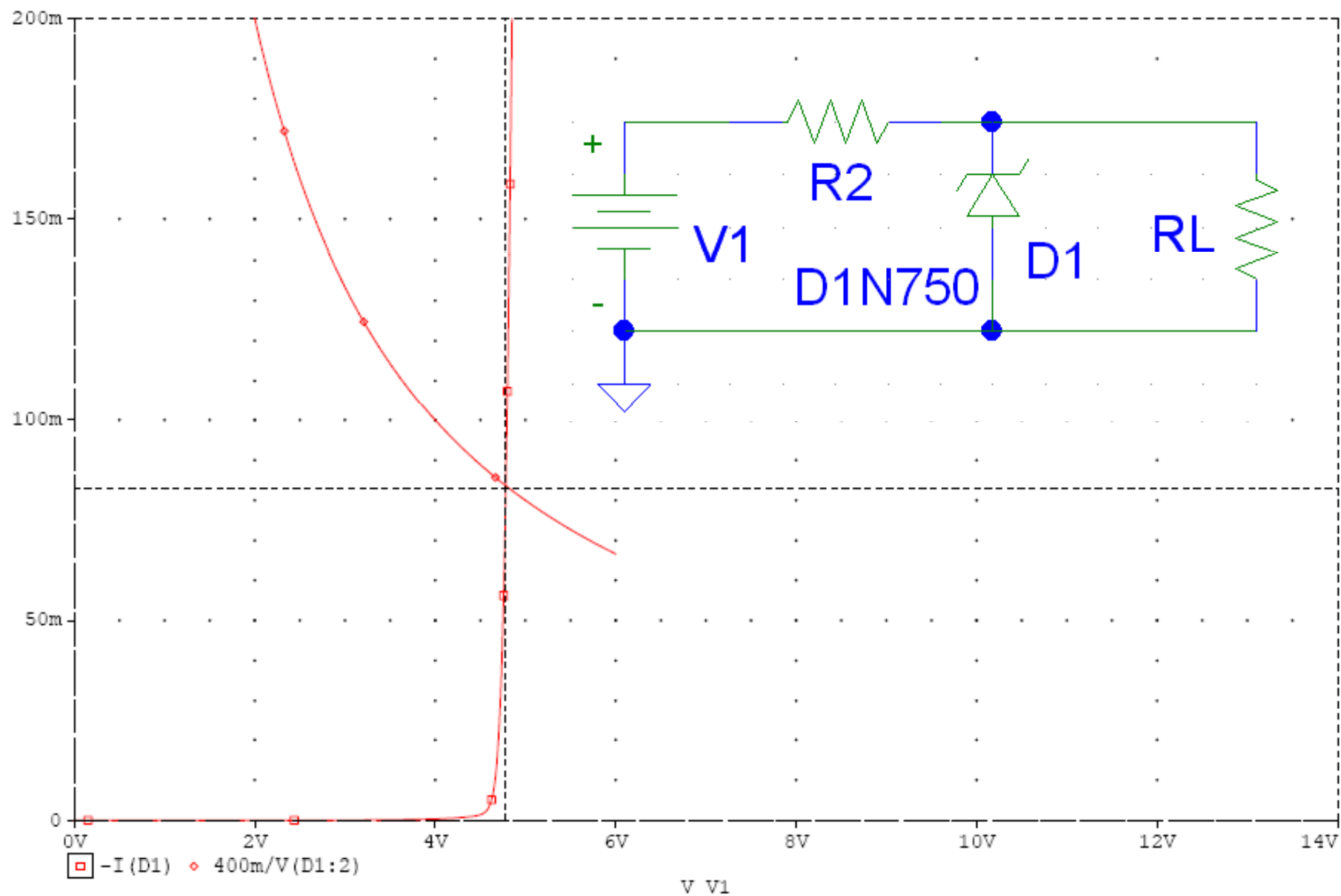

A1: (4.7815, 83.077m) A2: (0.000, -222.3E-18) DIFF(A): (4.7815, 83.077m)

Zener Diode Regulator Design

- $13.5 < V_1 < 14.5V$... range of auto system

$$\text{LL: } I_{\text{LL}} = \frac{V_{\text{Th}} - V_{\text{D,R}}}{R_{\text{Th}}}$$

$$\text{PWL: } I_{\text{D,R}} = \frac{V_{\text{D,R}} - \text{BV}}{r_{\text{Z}}}, \quad V_{\text{D,R}} > \text{BV}$$

- Should design for $P \leq P_{\text{D}} = 400 \text{ mW}$ (will use 90%). This usually means we can ignore the finite value of r_{z} , so $v_{\text{D}} = \text{BV}$, for $i_{\text{D}} > 0$.

Zener Regulator Design (cont.)

- The load line intercepts and slopes are


$$V_{Th} = V_1 \frac{R_L}{R_2 + R_L}$$

$$R_{Th} = \frac{R_2 R_L}{R_2 + R_L} \Rightarrow G_{Th} = \frac{R_2 + R_L}{R_2 R_L}$$

$$I_N = V_1 \frac{R_L}{R_2 + R_L} / \frac{R_1 R_L}{R_2 + R_L} = \frac{V_1}{R_2}$$

- $V_{Th,max} = V_{1,max}$ for $R_L \rightarrow \infty$, (open-cir.)
- R_2 is set for I_N such that at $V_1 = 14.5$
 $i_Z(BV) \cdot BV = 90\% PD = 360 \text{ mW}$
 $i_Z(BV) = 360 \text{ mW} / 4.7 \text{ V} = 76.6 \text{ mA}$

(A) ZenerChar.dat

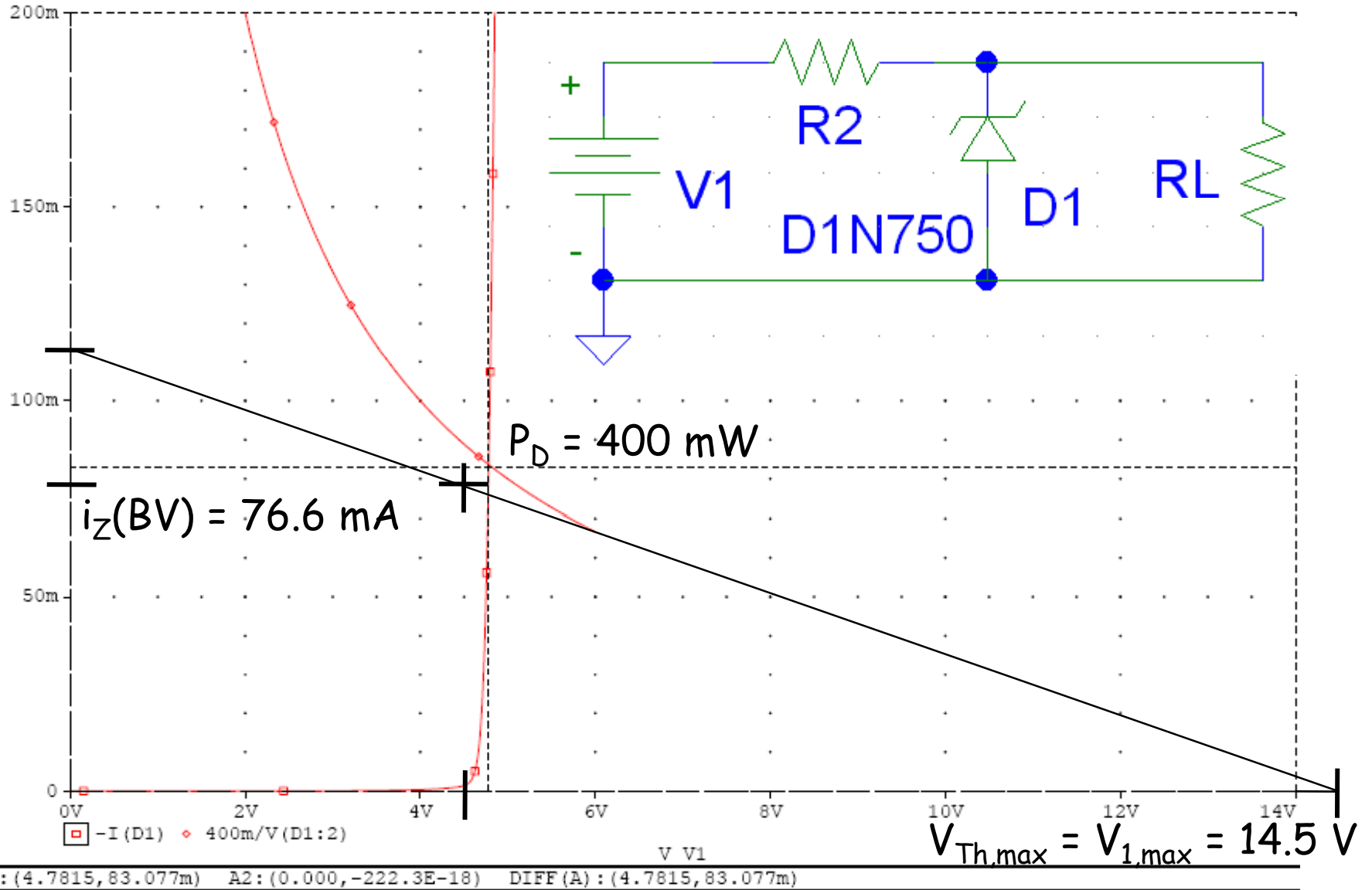

Zener Regulator Design (cont.)

- 76.6 mA at $v_Z = BV$ gives 90% PD
- For $V_{Th,max} = 14.5 = V_{1,max}$
- $113.33 \text{ mA} = I_N = V_1/R_2$
- $127.9 \text{ Ohm} = R_2 = V_1/I_n$
- 5% resistors are available at 120Ω and 130Ω . Which should be chosen? Why?
- What about P_{dmax} curve going below the load line?

Zener Regulator Design (cont.)

- What is the minimum value for R_L ?


Zener Regulator Design (cont.)

- What is V_{Th} for 13.5 V at R_{Lmin} ?

Zener Regulator Design (cont.)

- What is I_N for 13.5 V at R_{Lmin} ?

(A) ZenerCircuitComplete.dat

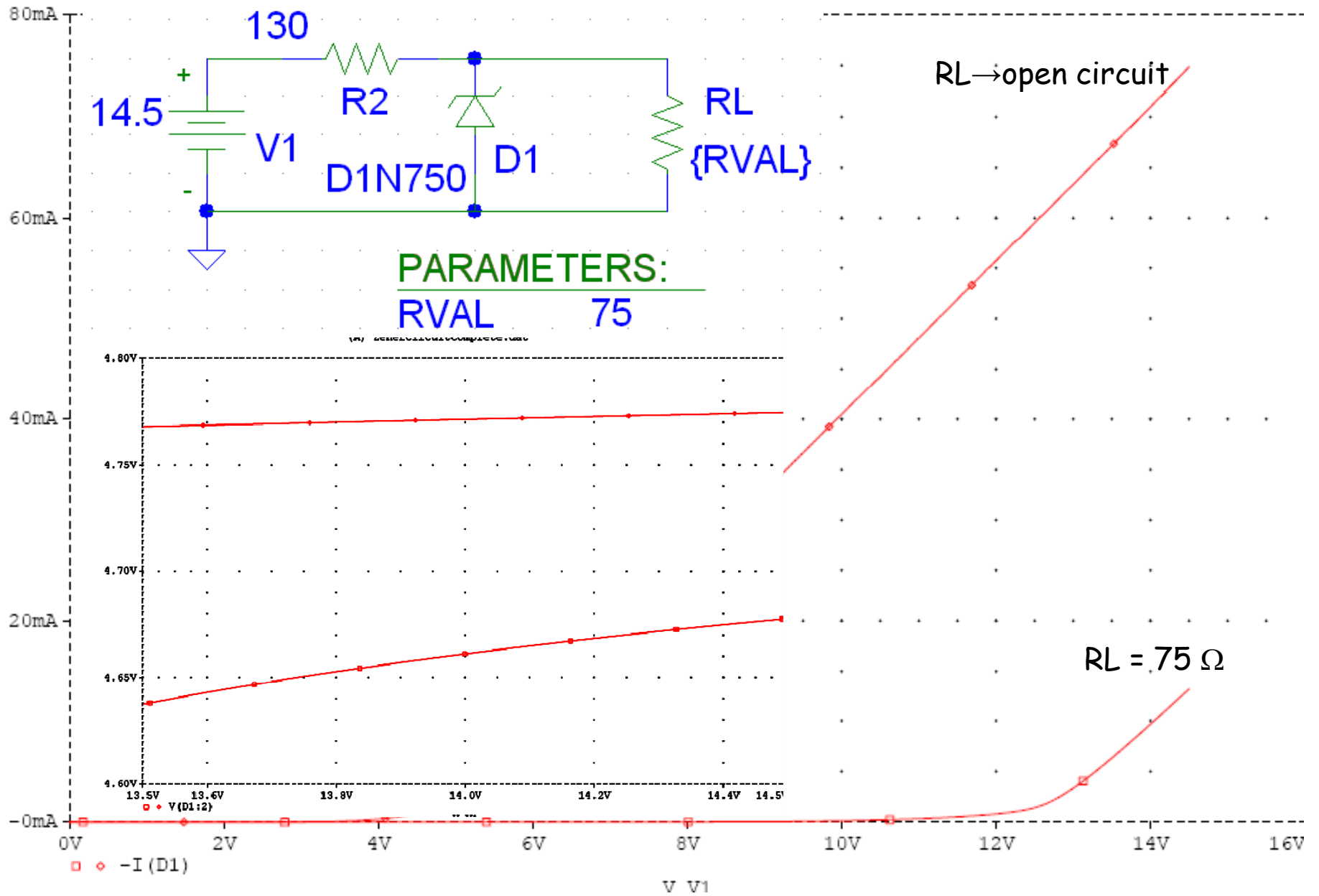

References and Endnotes

- Where not otherwise noted, Figures are taken from:
 - Electronics, 2nd edition, by Allan R. Hambley, Prentice Hall, Upper Saddle River, NJ, © 2000.
- (1) Microsim PSpice Reference Manual, Version 8.0, June, 1997. © 1997, MicroSim Corporation. [pspref.pdf]