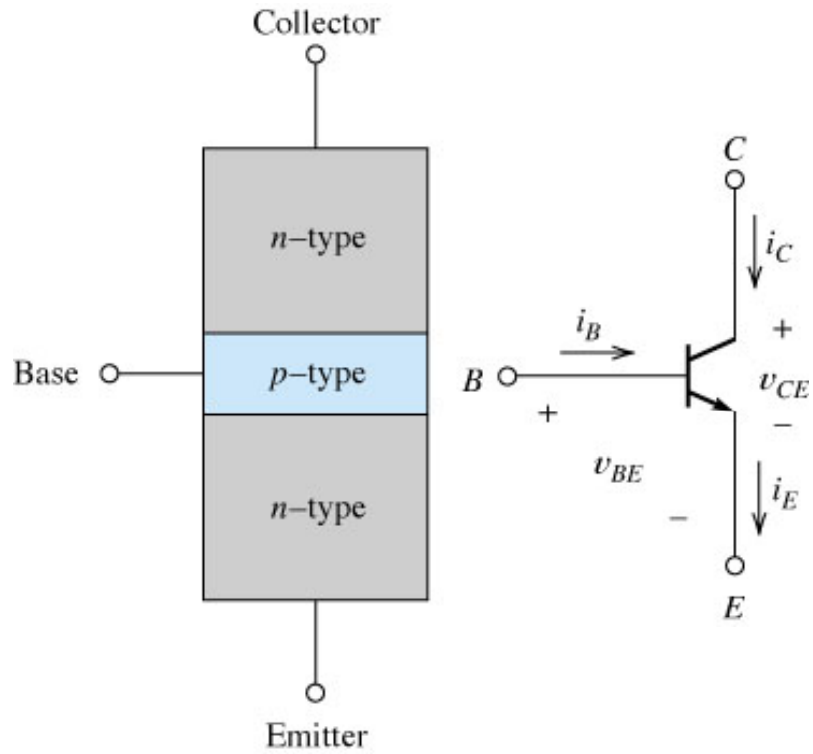



Lecture 22
EE 2303/001-Electronics I
April 13, 2009

Professor Ronald L. Carter
ronc@uta.edu
<http://www.uta.edu/ronc/>



(a) Simplified physical structure

Figure 4.1 The *npn* BJT.

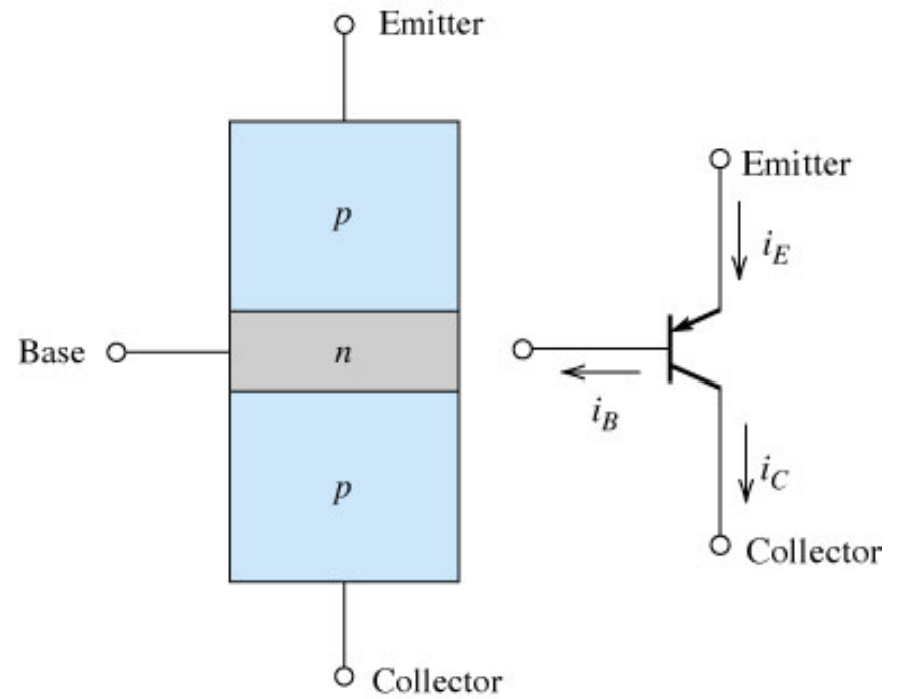

(a) Physical structure

Figure 4.16 The *pnp* BJT.



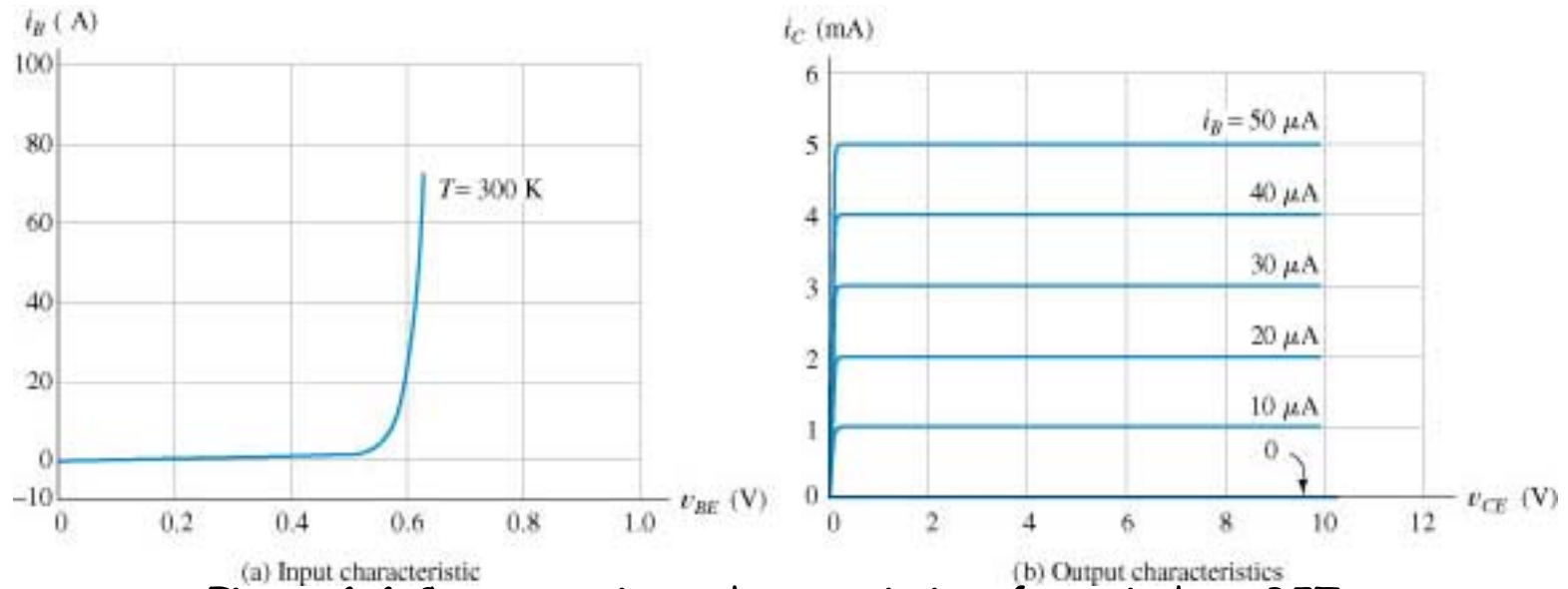


Figure 4.4 Common-emitter characteristics of a typical *nnp* BJT.

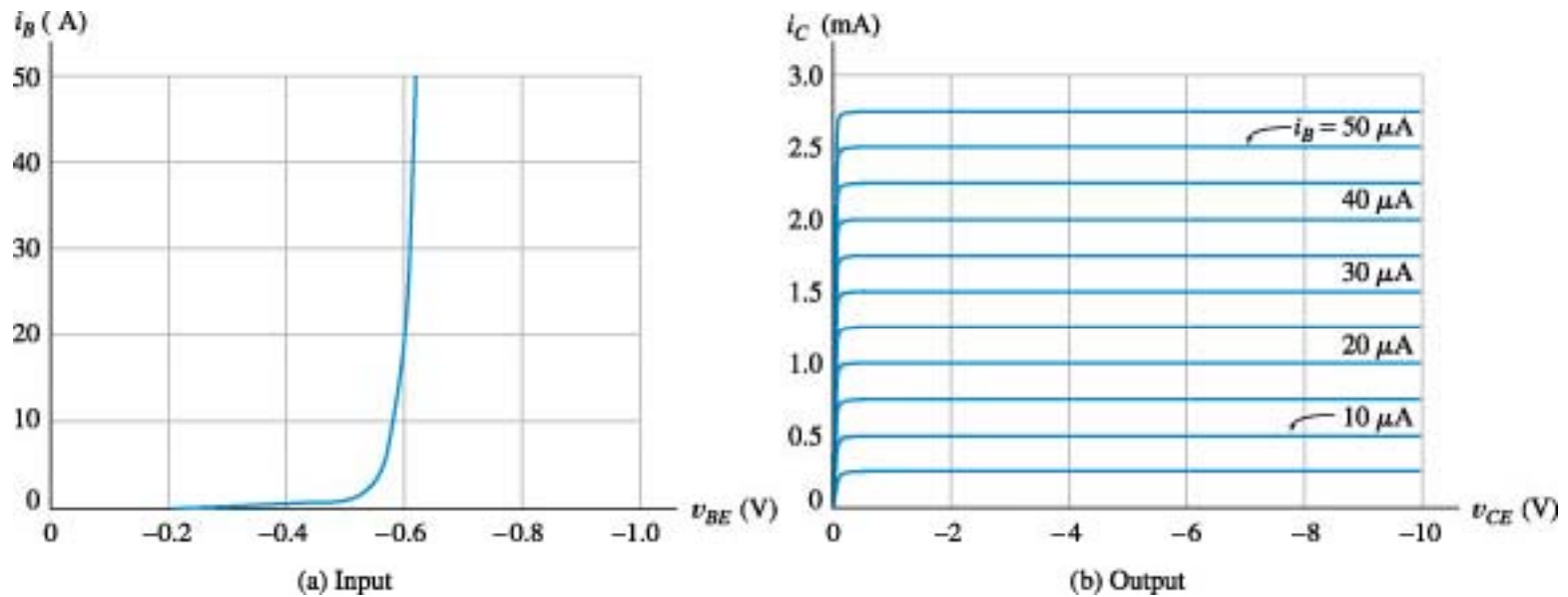

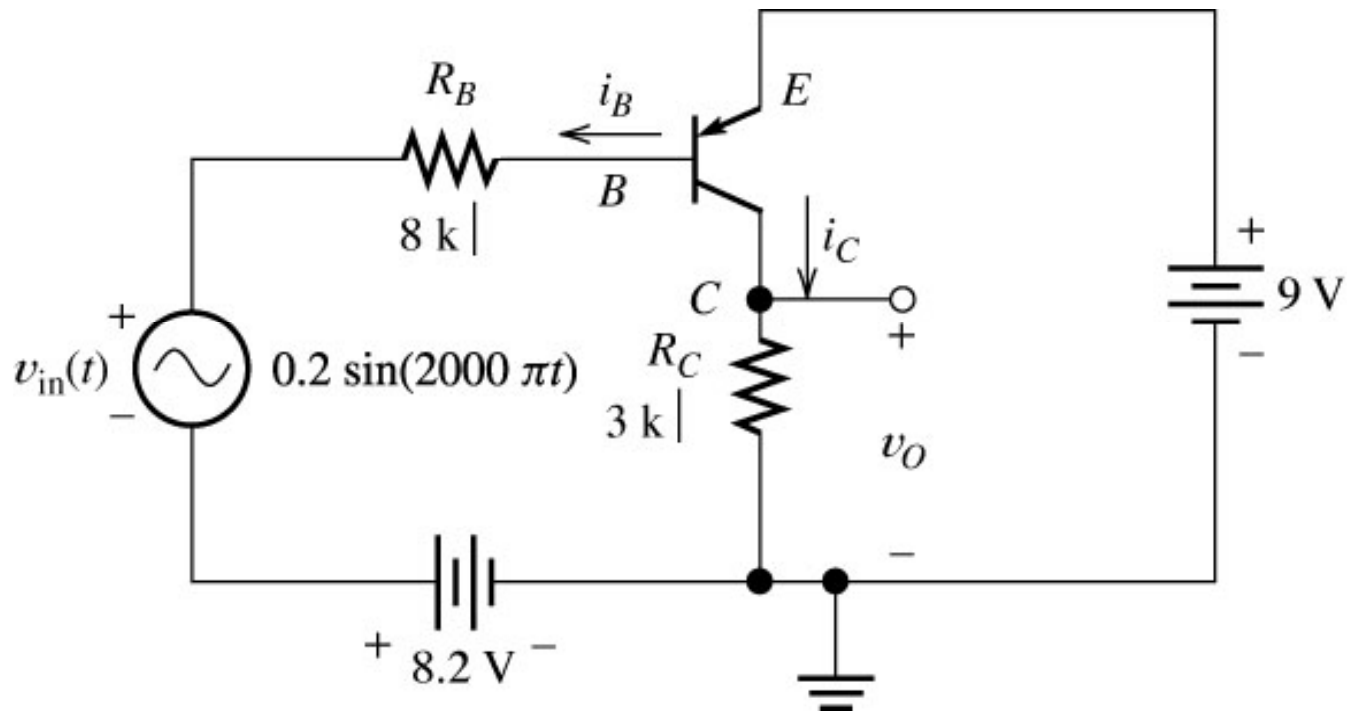L22 - 13Apr09 **Figure 4.17** Common-emitter characteristics for a *pnp* BJT.



L22 - 13Apr09 **Figure 4.18** Common-emitter amplifier for Exercise 4.8.

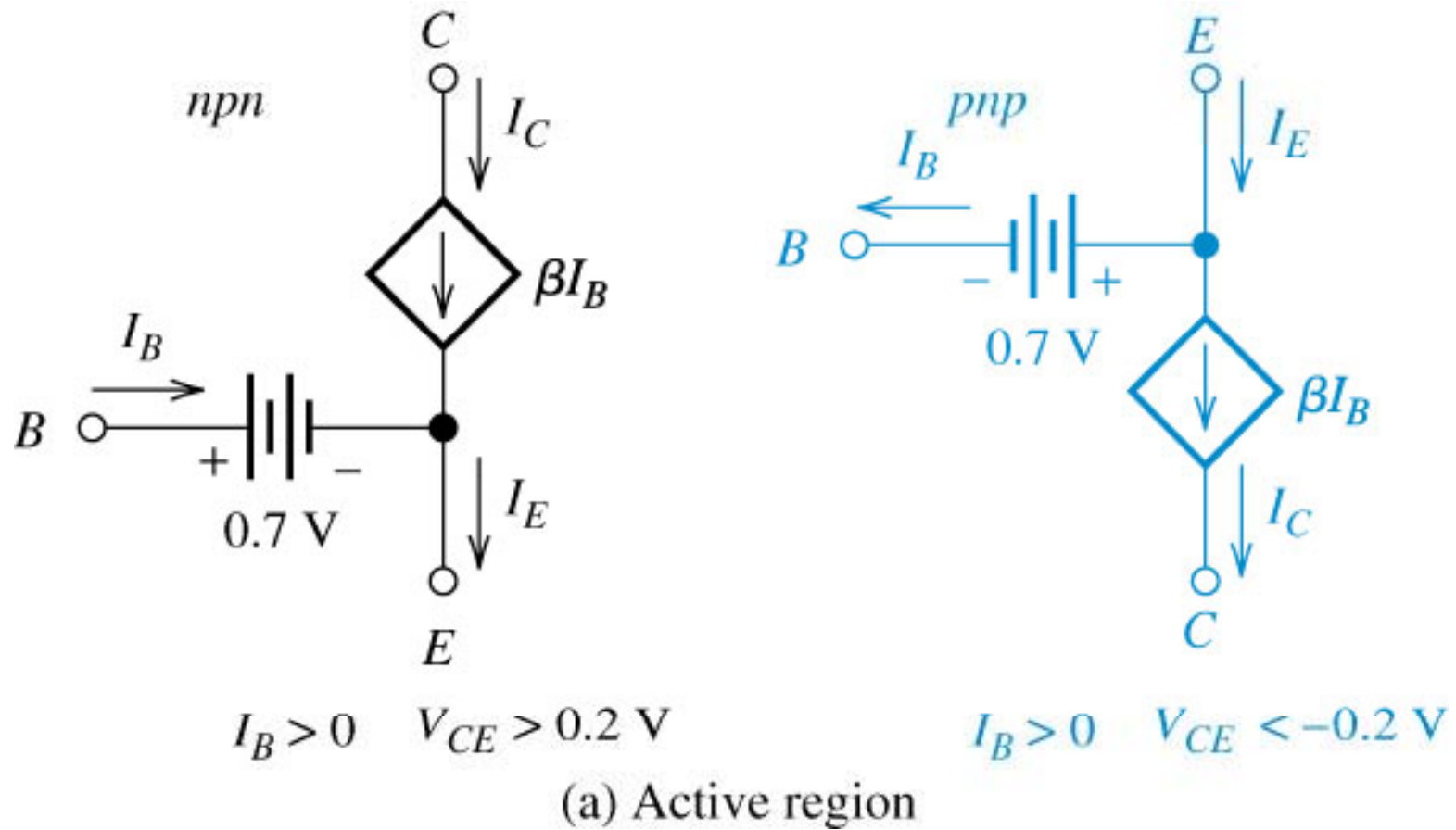


Figure 4.19a BJT large-signal models. (Note: Values shown are appropriate for typical small-signal silicon devices at a temperature of 300K.)

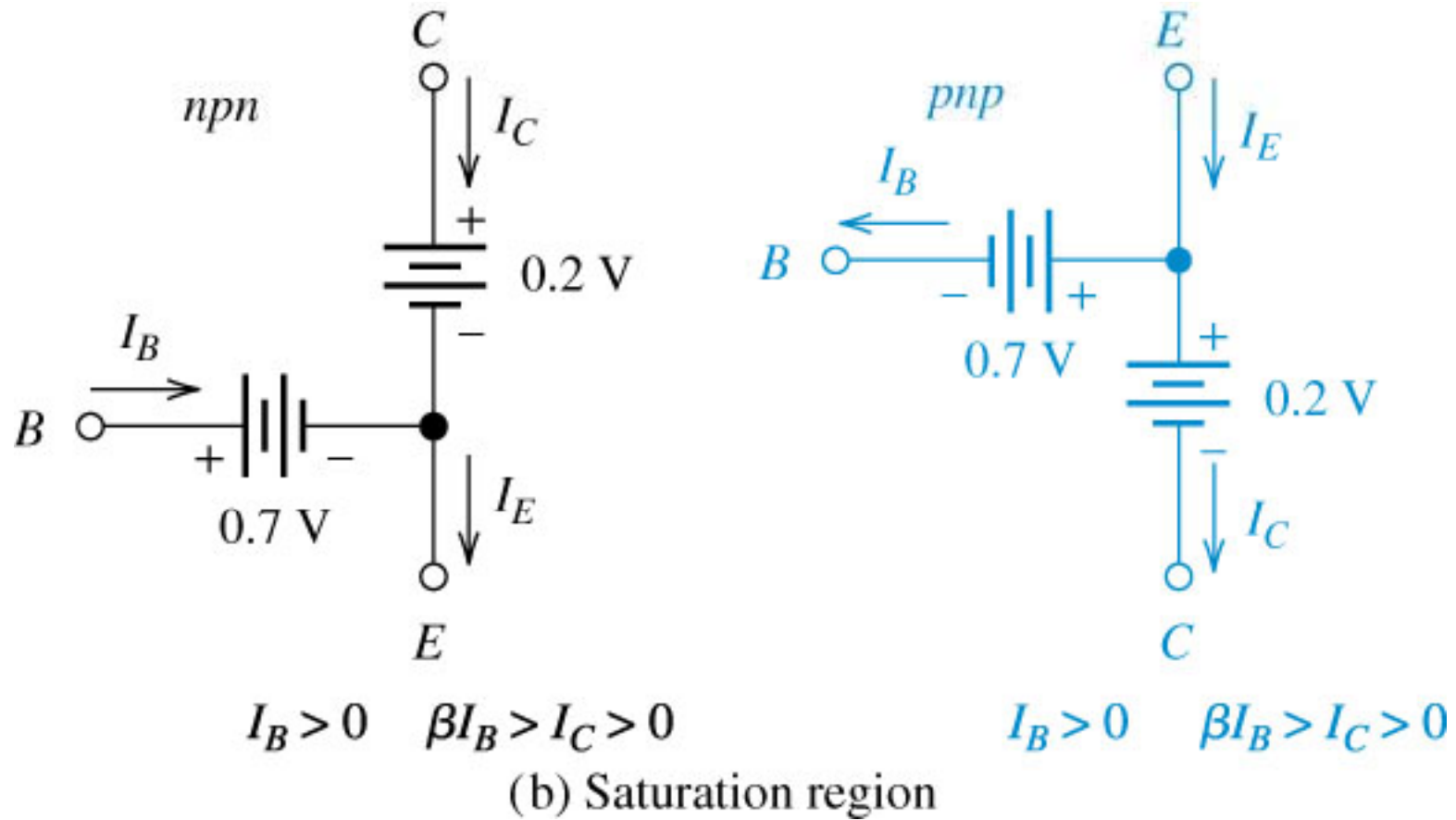


Figure 4.19b BJT large-signal models. (Note: Values shown are appropriate for typical small-signal silicon devices at a temperature of 300K.)




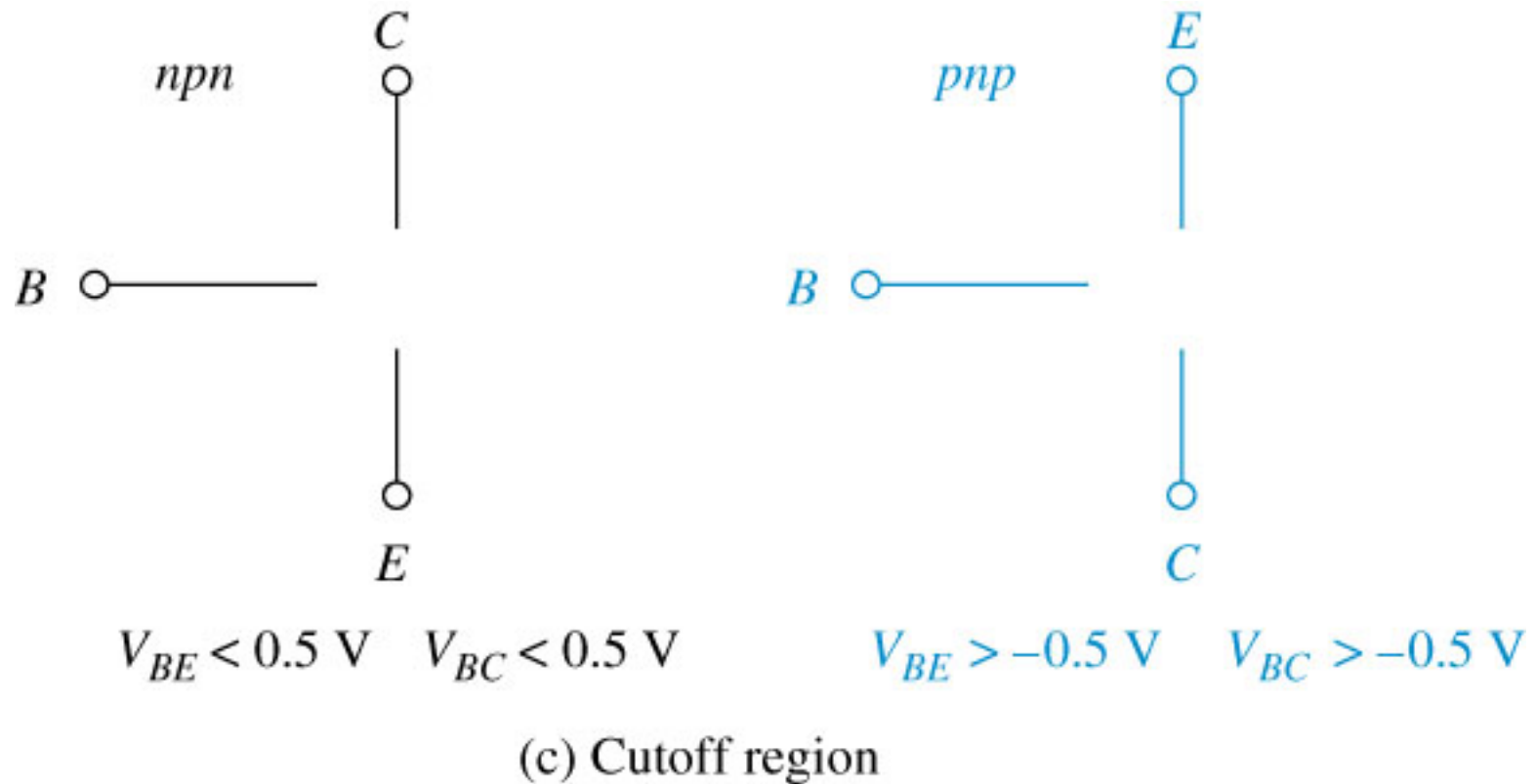


Figure 4.19c BJT large-signal models. (Note: Values shown are appropriate for typical small-signal silicon devices at a temperature of 300K.)

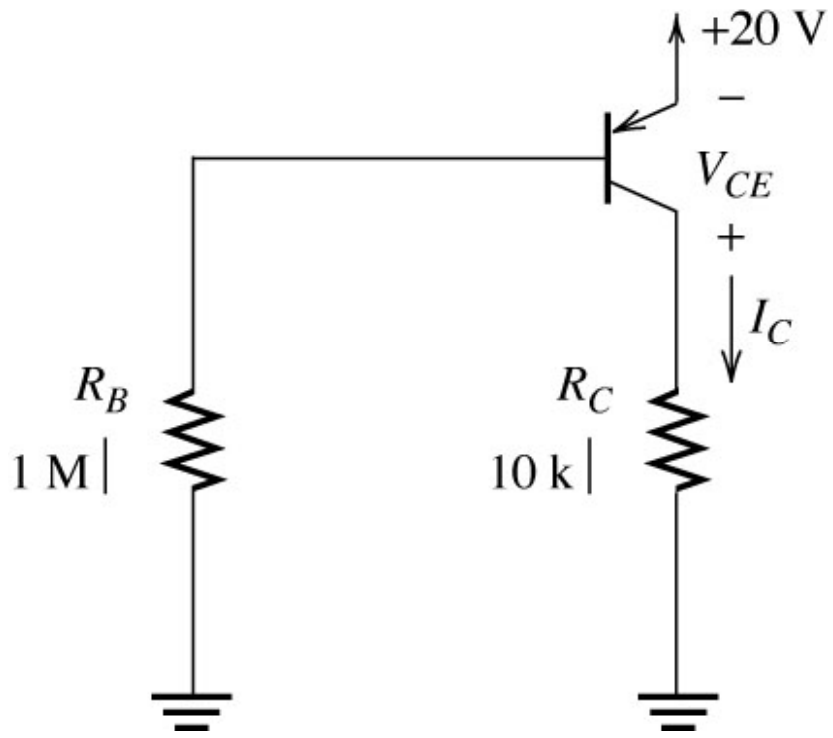

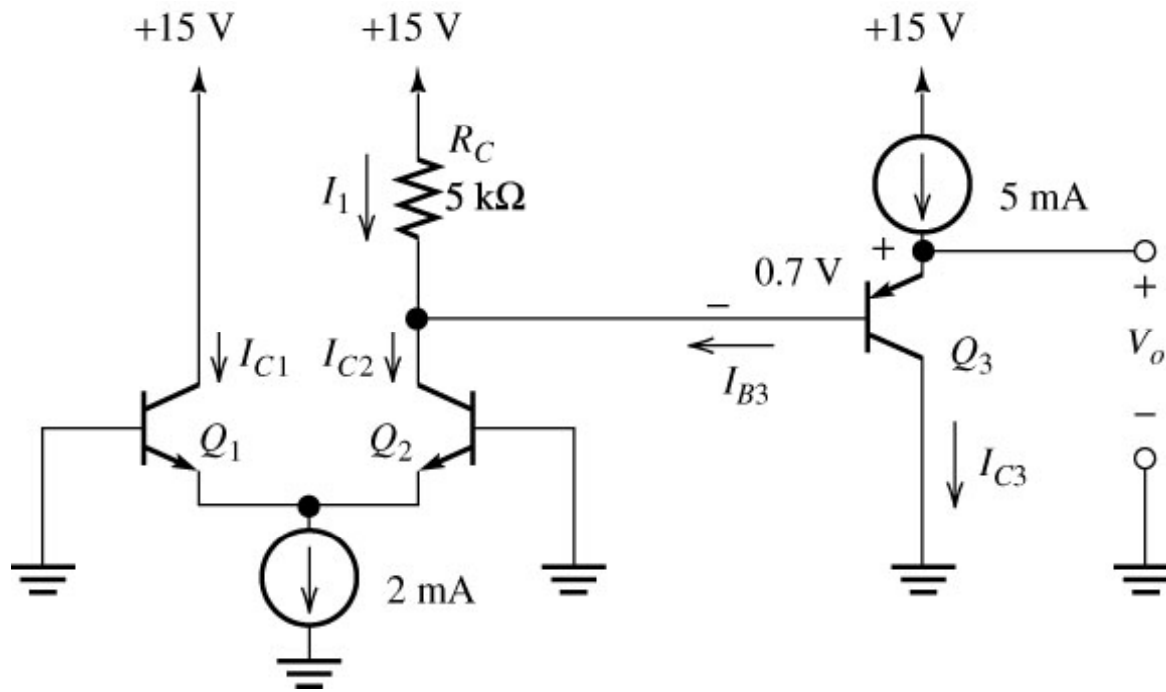

L22 - 13Apr09 **Figure 4.30** Current sources are useful in biasing IC amplifiers.

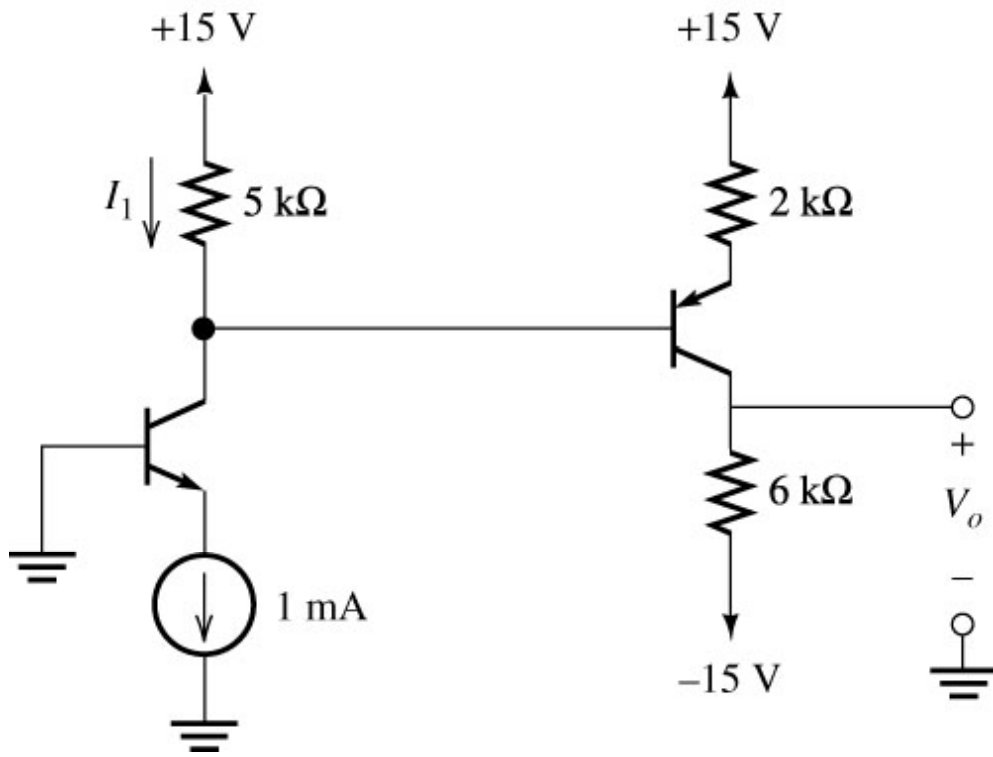



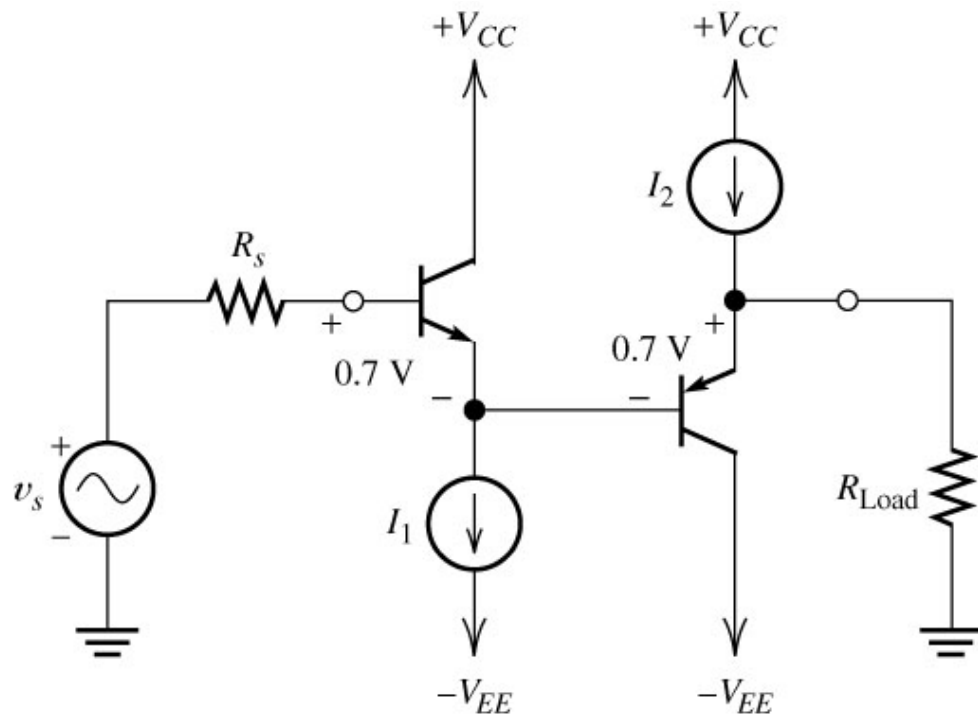


Figure 7.3 The offset voltage can be reduced by cascading a complementary (*pnp*) emitter follower.

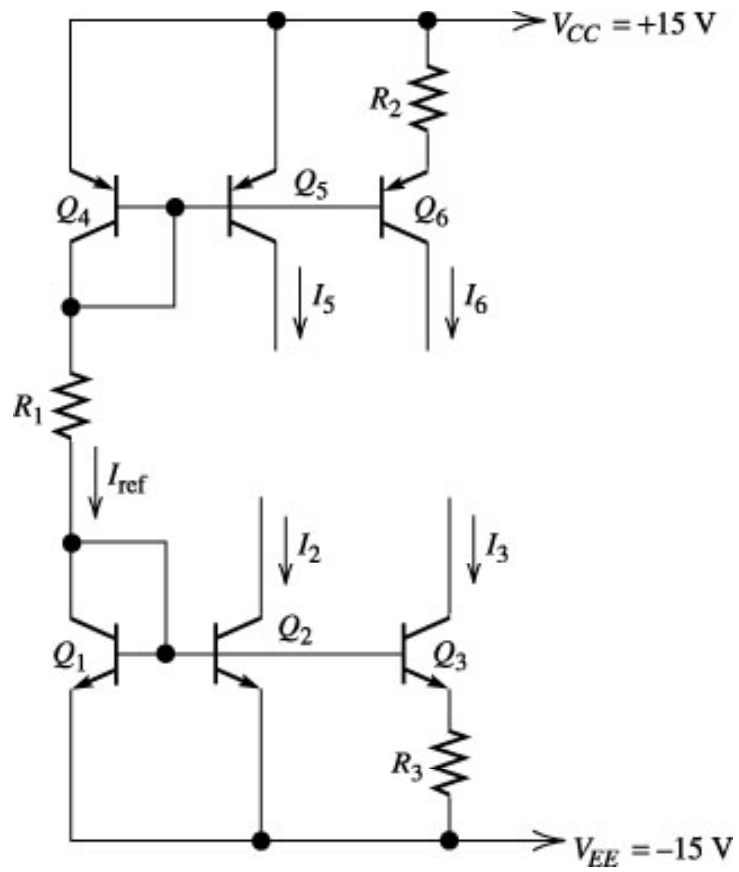

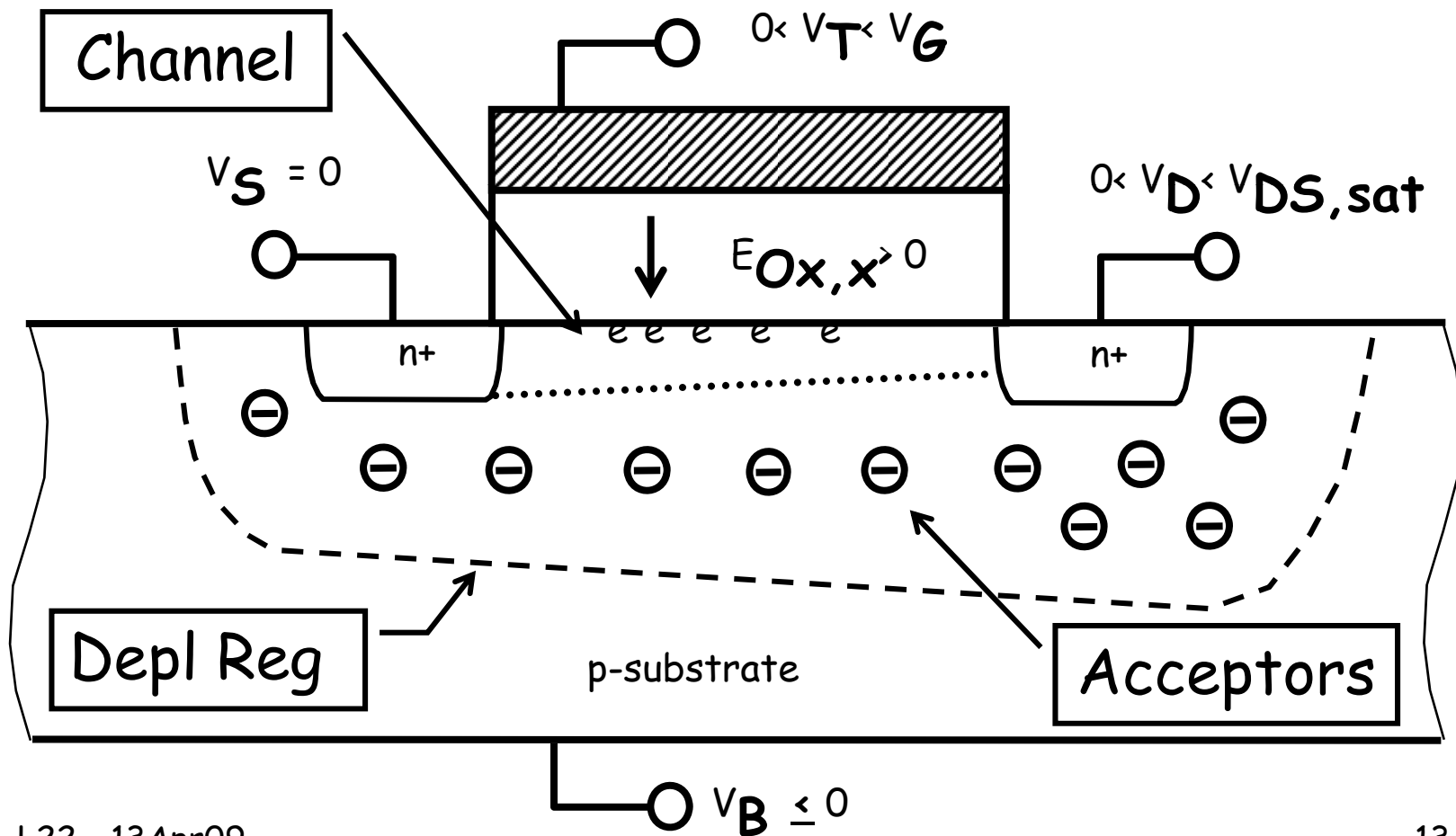n-channel enhancement MOSFET in ohmic region



Conductance of inverted channel

- $Q'_n = -C'_{ox}(V_{GC} - V_T)$
- $n'_s = C'_{ox}(V_{GC} - V_T)/q$, (# inv elect/cm²)
- The conductivity $\sigma_n = (n'_s/t) q \mu_n$
- $G = \sigma_n(Wt/L) = n'_s q \mu_n (W/L) = 1/R$, so
- $I = V/R = dV/dR$, $dR = dL/(n'_s q \mu_n W)$

$$I \int_0^L dL = \int_{V_S}^{V_D} C'_{ox} ((V_G - V_C) - V_T) \mu_n W dV$$

Basic I-V relation for MOS channel

$$I_D = \frac{W\mu_n C_{Ox}}{2L} (2(V_G - V_T)V_{DS} - V_{DS}^2), \quad V_{DS} < V_G - V_T$$

At $V_{DS} = V_{DS,sat} = V_G - V_T$, $Q'_n(y=L) = 0 \Rightarrow \text{Sat.}$

so let I_D be given by $I_D(V_{DS,sat})$,

for $V_{DS} > V_{DS,sat} = V_G - V_T$ so

$$I_D = I_{D,sat} = \frac{W\mu_n C_{Ox}}{2L} (V_G - V_T)^2$$

I-V relation for n-MOS (ohmic reg)

$$I_D = \frac{\mu_n C'_{ox}}{2} \frac{W}{L} (2(V_G - V_T)V_{DS} - V_{DS}^2). \text{ Note for}$$

$$V_{DS} \geq V_G - V_T = V_{DS,sat},$$


result is non-physical.

At $V_{DS,sat}$, $n'_{s,y=L} = 0$

assume that channel curr.

is const for $V_{DS} \geq V_{DS,sat}$

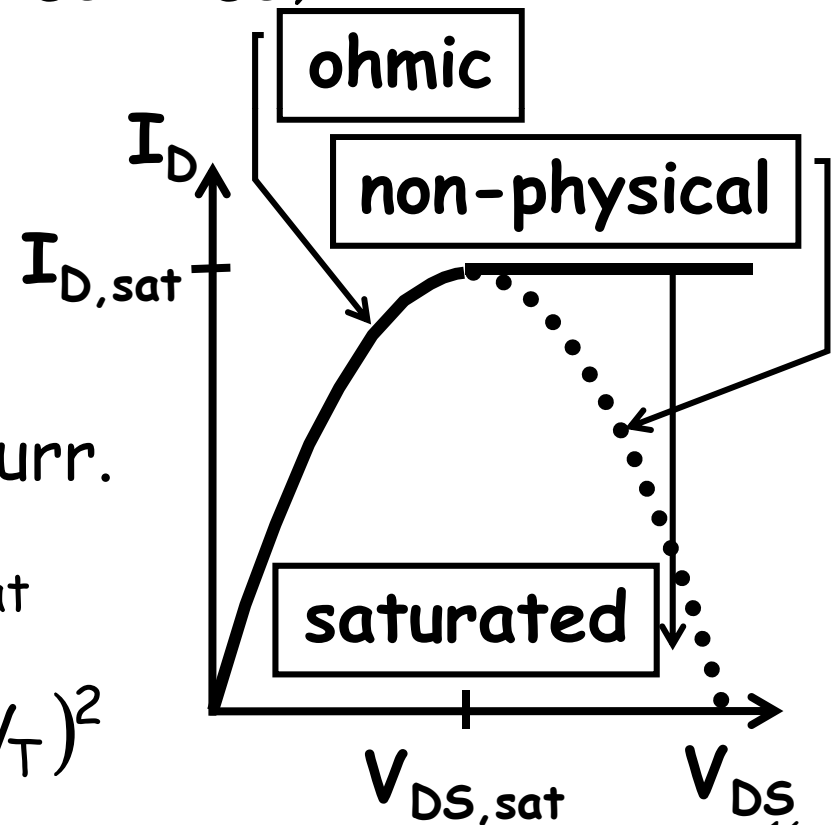
$$I_{D,sat} = \frac{\mu_n C'_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2$$




Universal drain characteristic

$$I_{D1} = \frac{\mu_n C'_{Ox}}{2} \frac{W}{L} \times (1V)^2$$
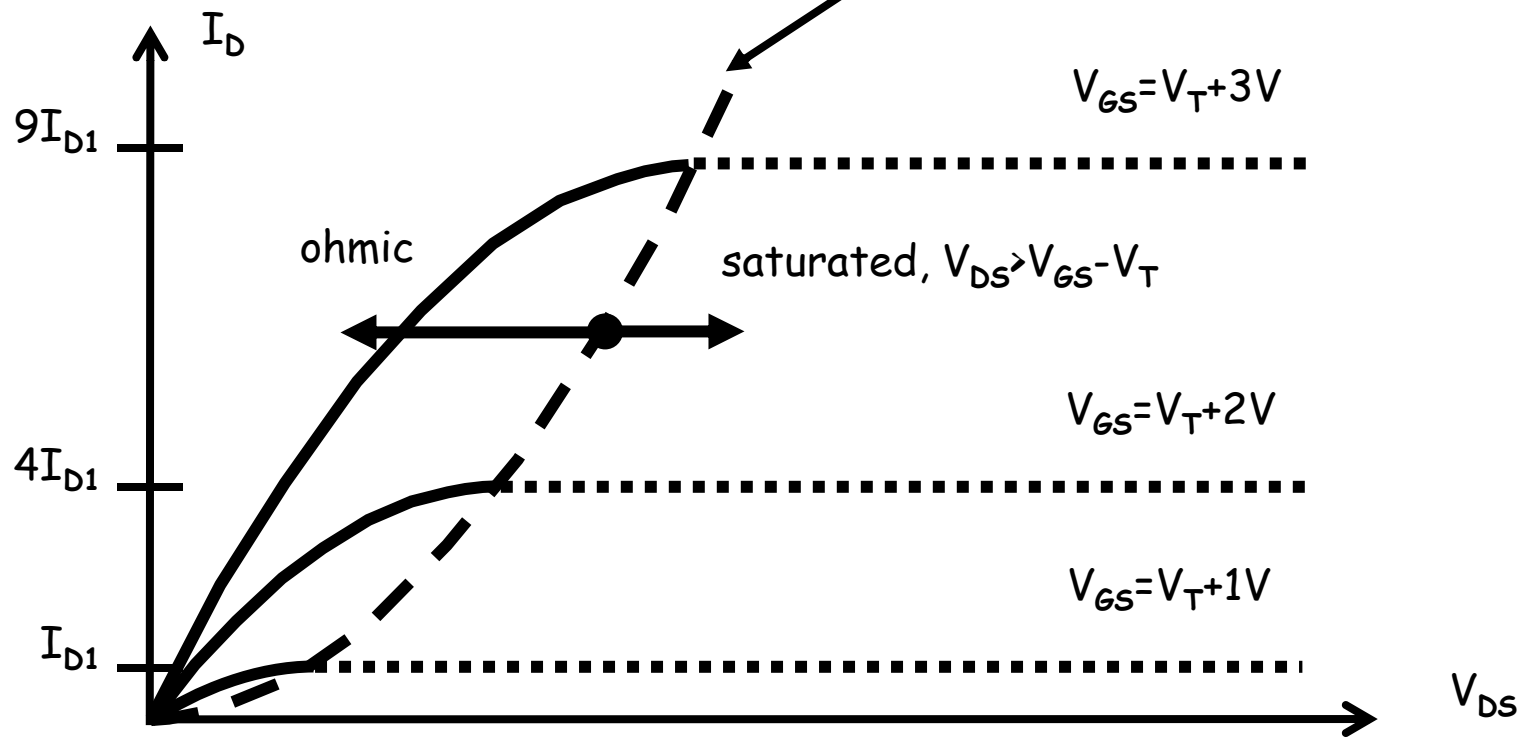
$$I_{D,sat} = \frac{\mu_n C'_{Ox}}{2} \frac{W}{L} V_{DS}^2$$




Characterizing the n-ch MOSFET

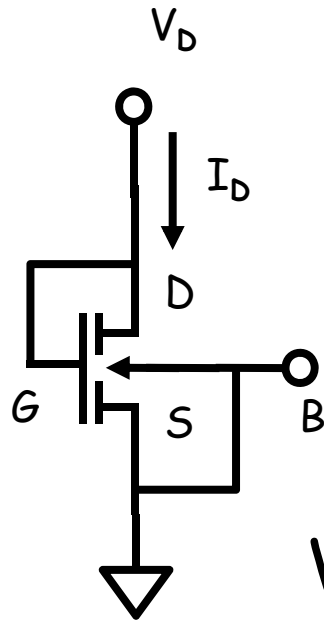

$$V_{DS} = V_{GS}, \quad V_T \geq 0$$

$$V_{DS} \geq V_{GS} - V_T, \text{ so}$$
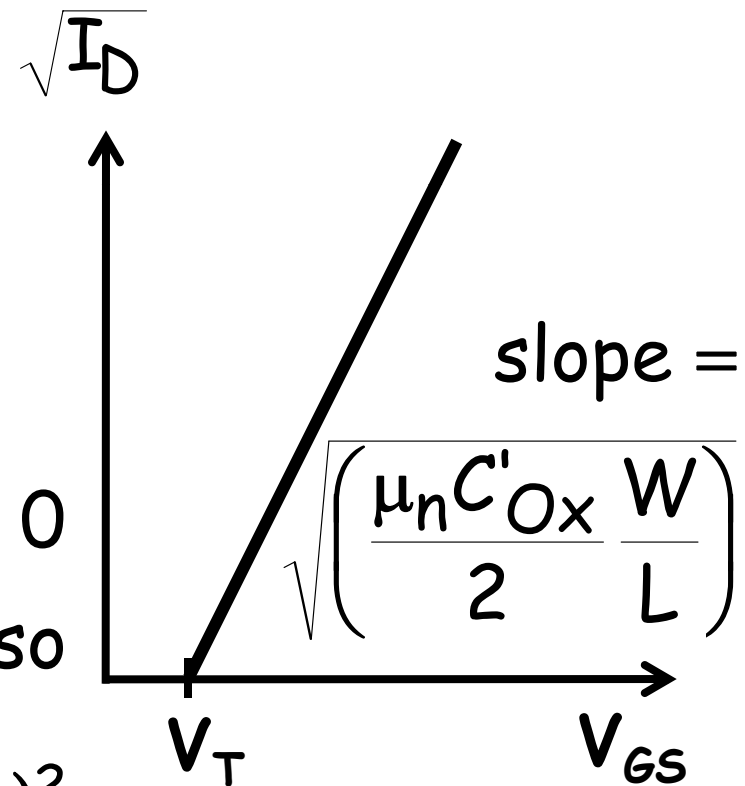
$$I_{D,sat} = \frac{\mu_n C'_{Ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2$$



Low field ohmic characteristics

$$I_D = \frac{\mu_n C'_{Ox}}{2} \frac{W}{L} (2(V_{GS} - V_T)V_{DS} - V_{DS}^2),$$

for ohmic region. Furthermore, let

$V_{DS} \ll V_G - V_T$, so that

$$I_D \approx \mu_n C'_{Ox} \frac{W}{L} (V_{GS} - V_T)V_{DS}$$

$$= KP \frac{W}{L} (V_{GS} - V_T)V_{DS}, \quad KP = \mu_n C'_{Ox}$$

$$\left[\frac{dI_D}{dV_{GS}} \right]_{V_{DS} \ll V_G - V_T} \approx KP \frac{W}{L} V_{DS}$$

MOSFET circuit parameters

Transconductance

$$g_m \equiv \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DS}}$$

$$g_{ms} = \frac{W \mu_n C'_{ox}}{L} V_{DS}, \text{ saturation}$$

$$g_{mL} = \frac{W \mu_n C'_{ox}}{L} (V_{GS} - V_T), \text{ ohmic region}$$

MOSFET circuit parameters (cont)

Output or drain conductance

$$g_d \equiv \left. \frac{\partial I_D}{\partial V_{DS}} \right|_{V_{GS}}$$

$$g_{ds} = 0, \text{ saturation}$$

$$g_{dL} = \frac{W \mu_n C'_{ox}}{L} (V_{GS} - V_T - V_{DS}), \text{ ohmic}$$

Substrate bias effect on V_T (body-effect)


Letting V_T calculation be relative to Source

$$V_T - V_S = V_{FB} - 2|\phi_p| - \frac{qN_a x_{d,max}}{C'_{ox}}, \text{ where}$$

$$x_{d,max} = \sqrt{\frac{2\varepsilon(2|\phi_p| + V_{SB})}{qN_a}}, \text{ so } \Delta V_T = V_T(V_{SB}) -$$

$$V_T(V_{SB} = 0) = \frac{\sqrt{2\varepsilon_{si}qN_a}}{C'_{ox}} \left(\sqrt{2|\phi_p| + V_{SB}} - \sqrt{2|\phi_p|} \right)$$

Body effect data

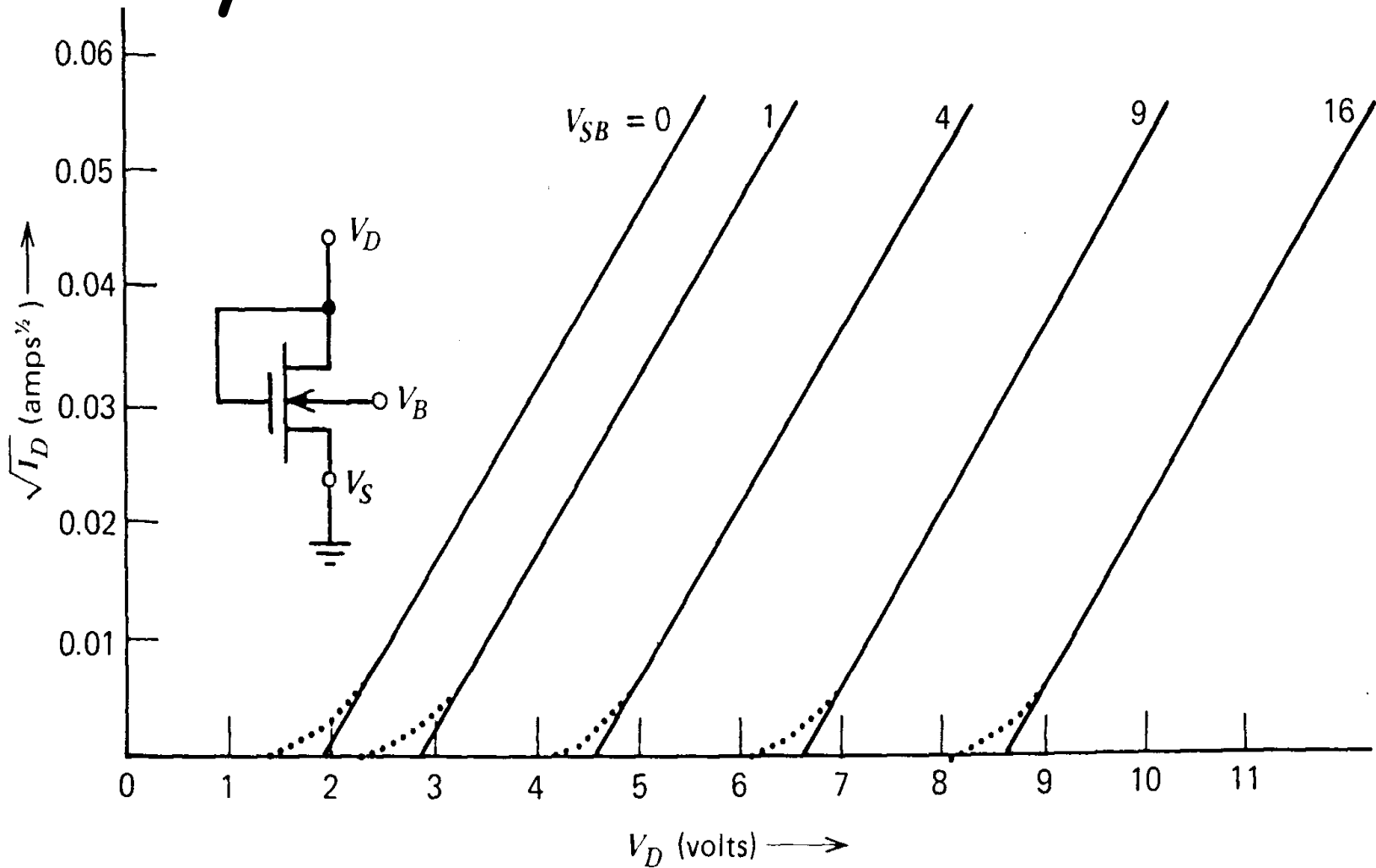

References and Endnotes

- Where not otherwise noted, figures with a figure number (e.g., Fig 3.2) are taken from:
 - Electronics, 2nd edition, by Allan R. Hambley, Prentice Hall, Upper Saddle River, NJ, © 2000.