
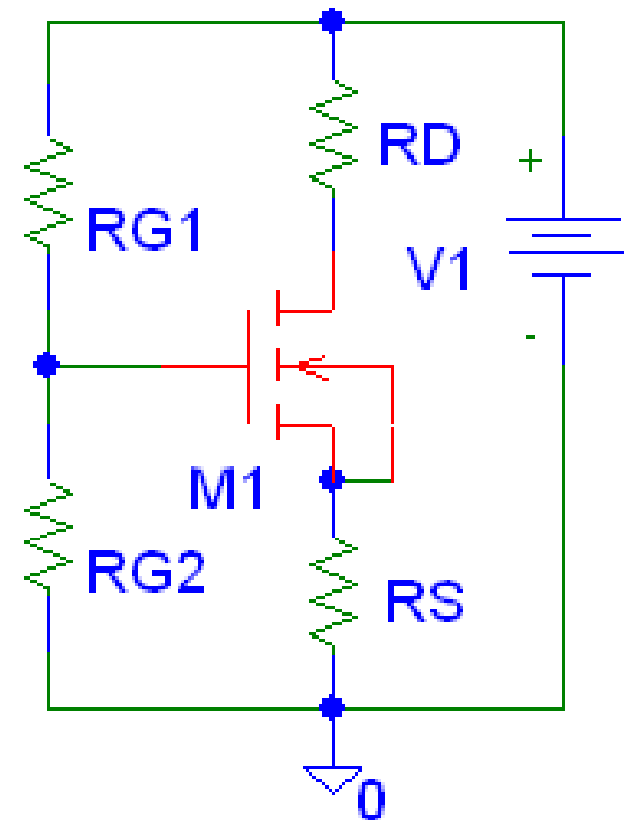


Lecture 26
EE 2303/001-Electronics I
April 27, 2009

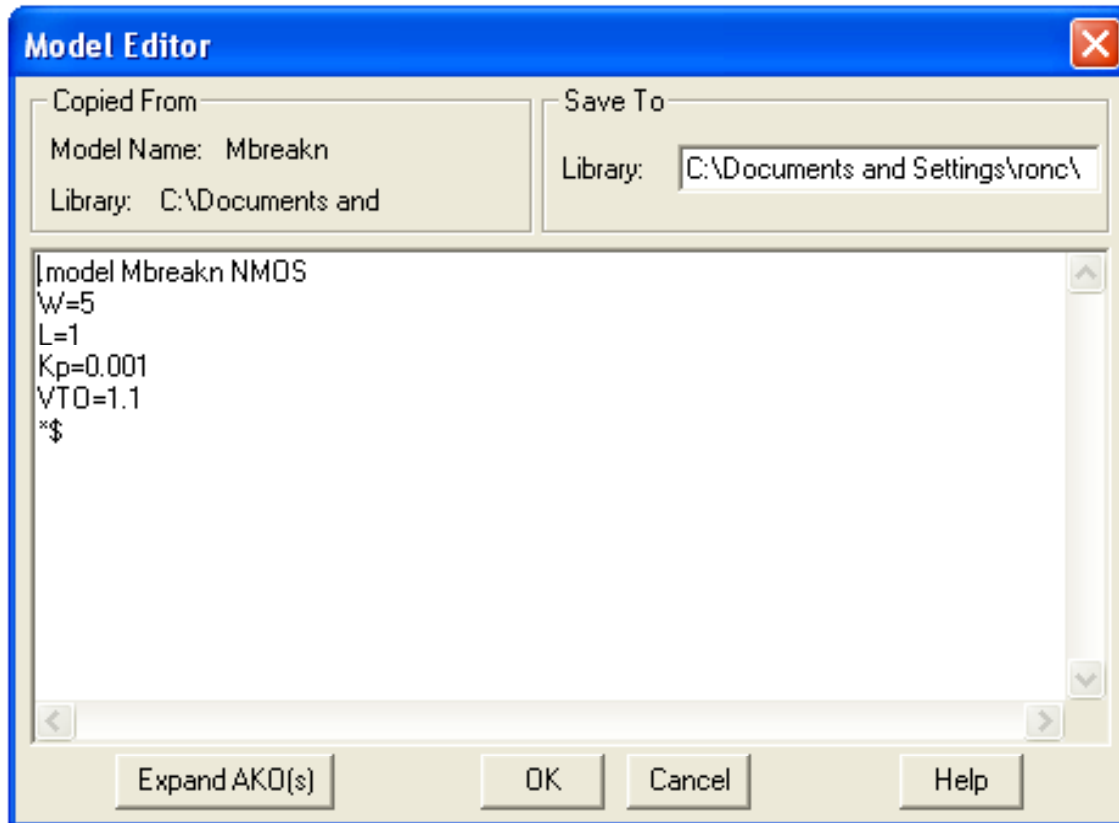
Professor Ronald L. Carter
ronc@uta.edu
<http://www.uta.edu/ronc/>



$$KP = \mu C'_{Ox}, \quad \mu = \text{carrier mobility}, \quad C'_{Ox} = \frac{\epsilon_{Ox}}{x_{Ox}}$$


$$K = \frac{KP}{2} \frac{W}{L}$$

L26 - 27Apr09

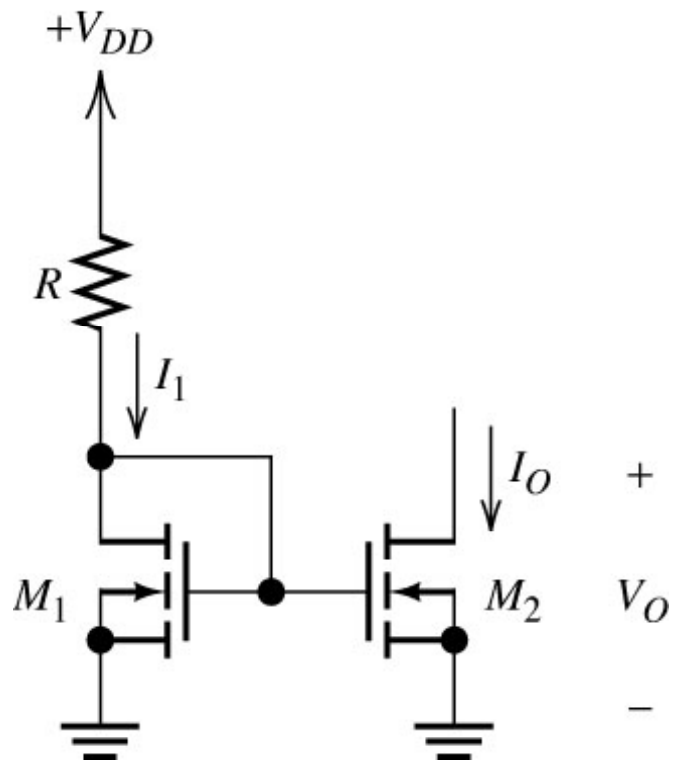




L26 - 27Apr09

Figure 7.15 NMOS current mirror.

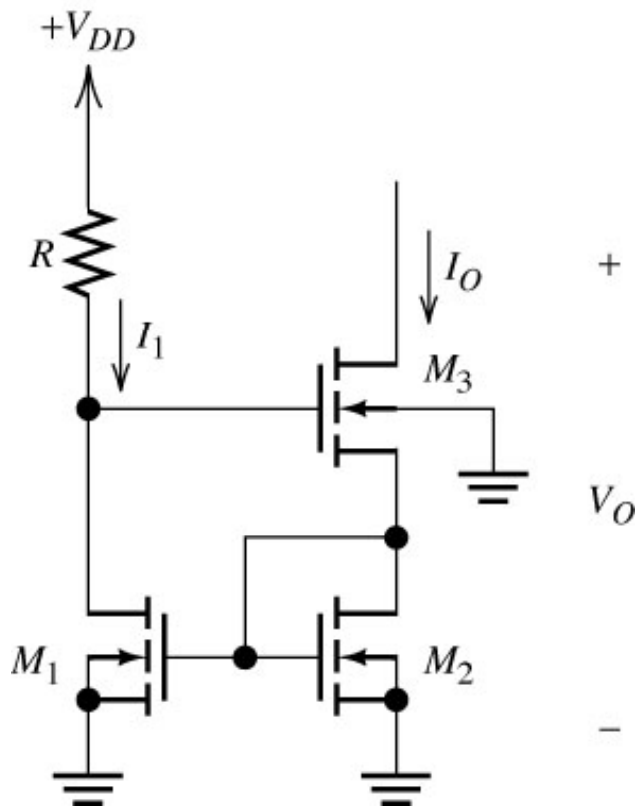


L26 - 27Apr09

Figure 7.16 NMOS Wilson current source.

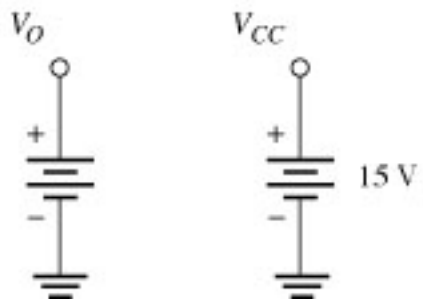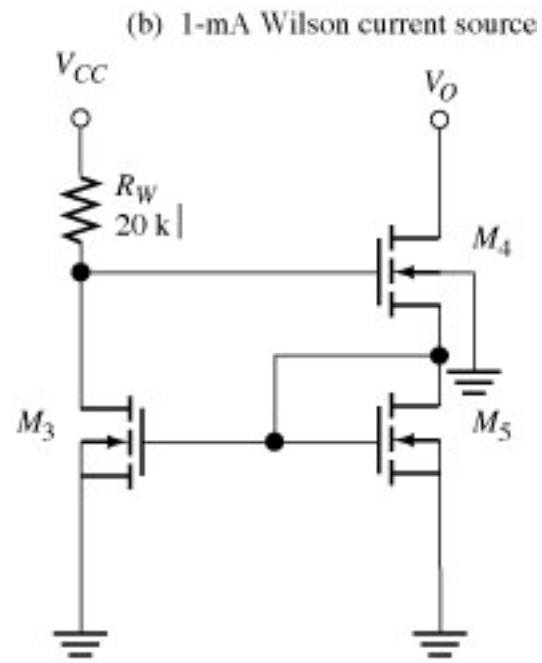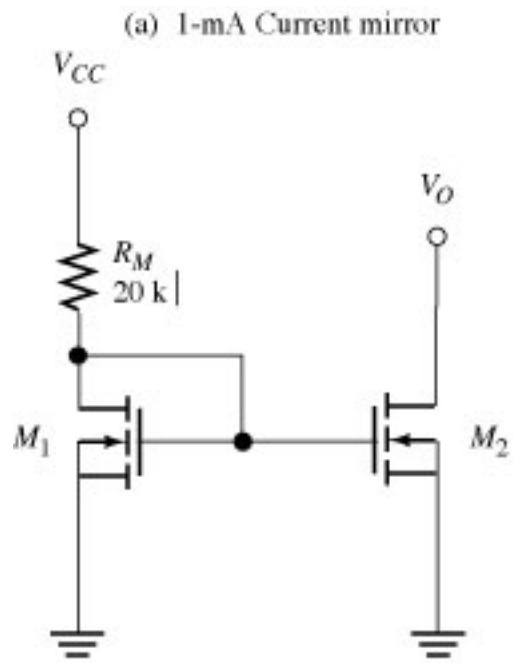


L26 - 27Apr09

Figure 7.17 Circuits for Exercise 7.4.

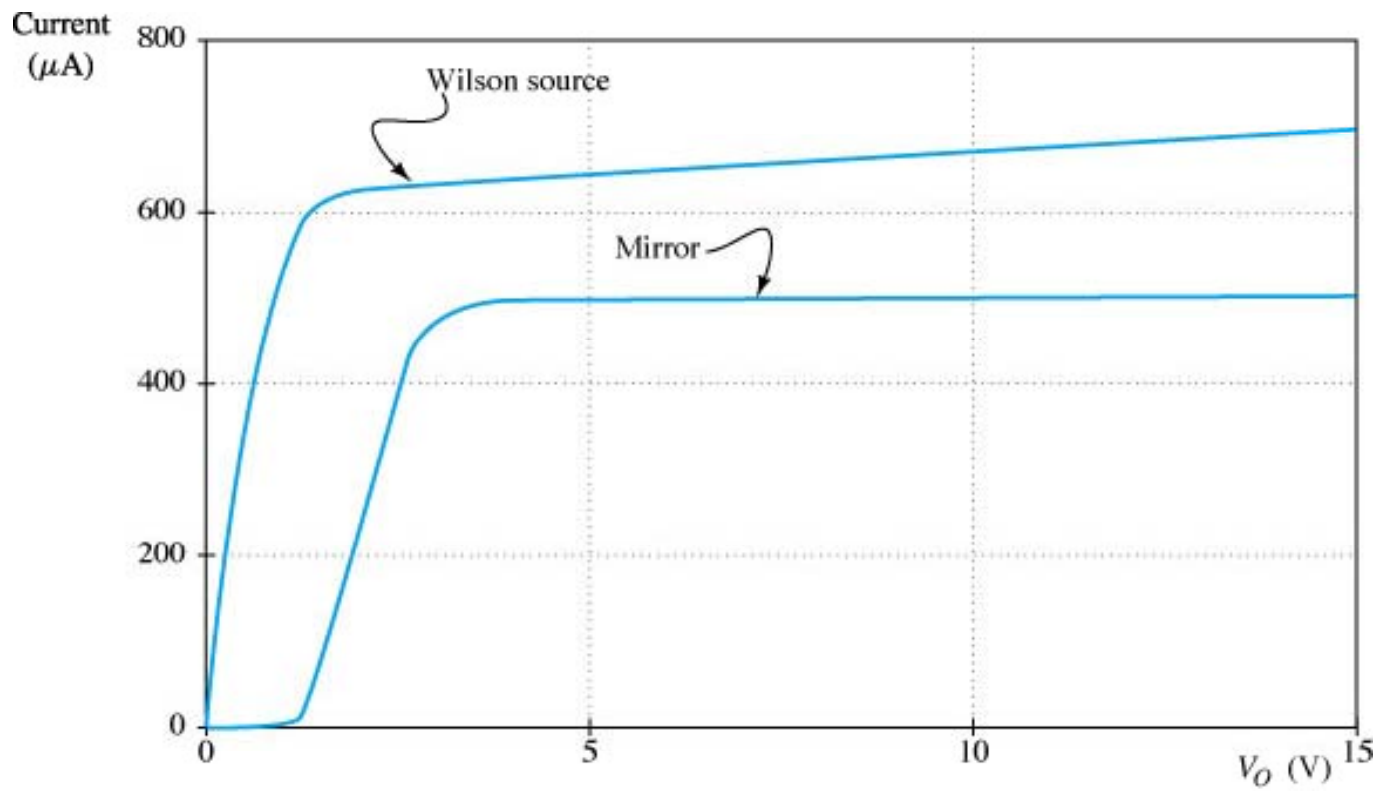


L26 - 27Apr09

Figure 7.18 Current versus voltage for the circuits of Figure 7.17.

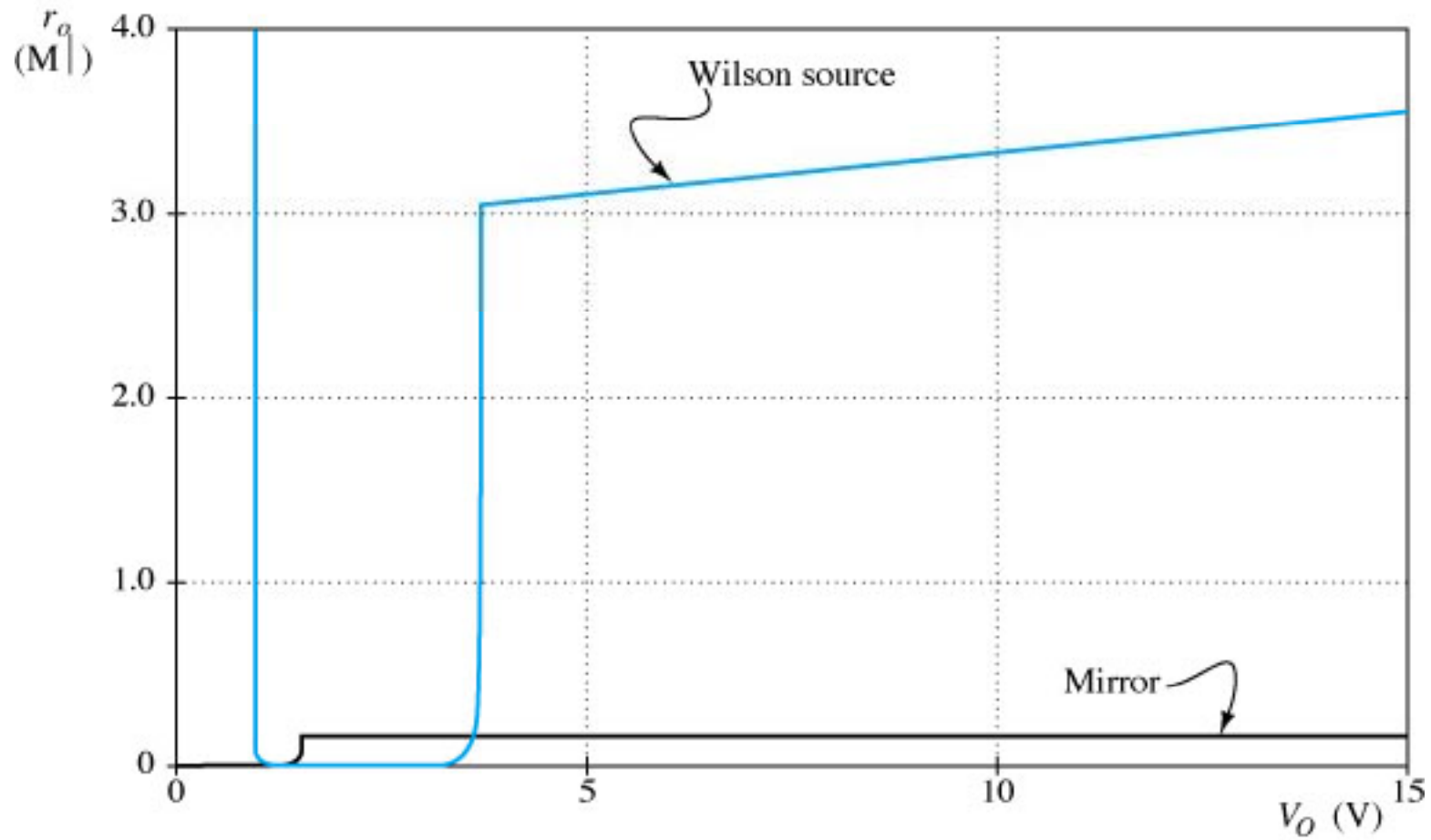


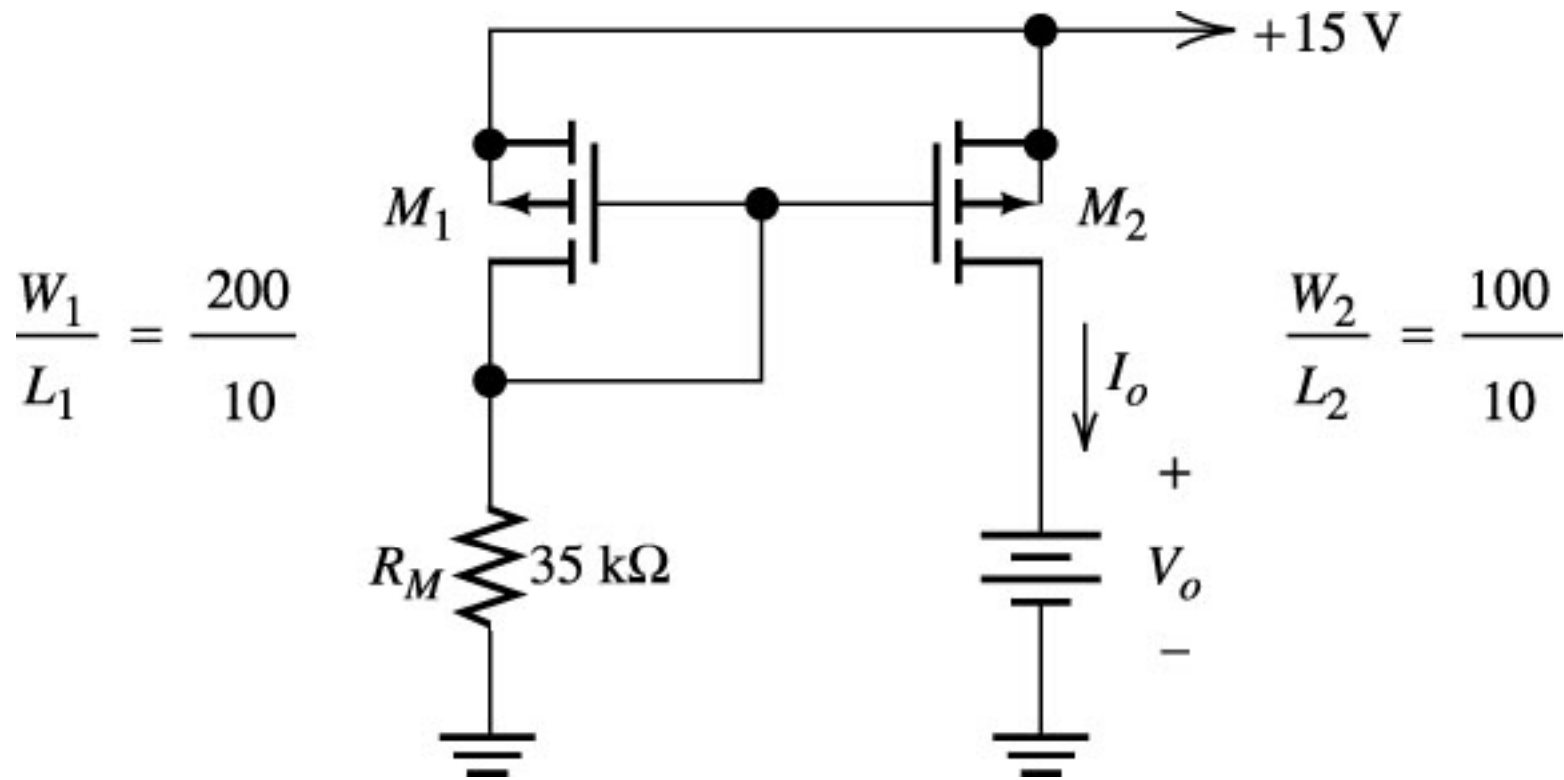L26 - 27Apr09 **Figure 7.19** Dynamic resistance versus voltage for the circuits of Figure 7.17.



L26 - 27Apr09


Figure 7.20 One solution for Exercise 7.7.

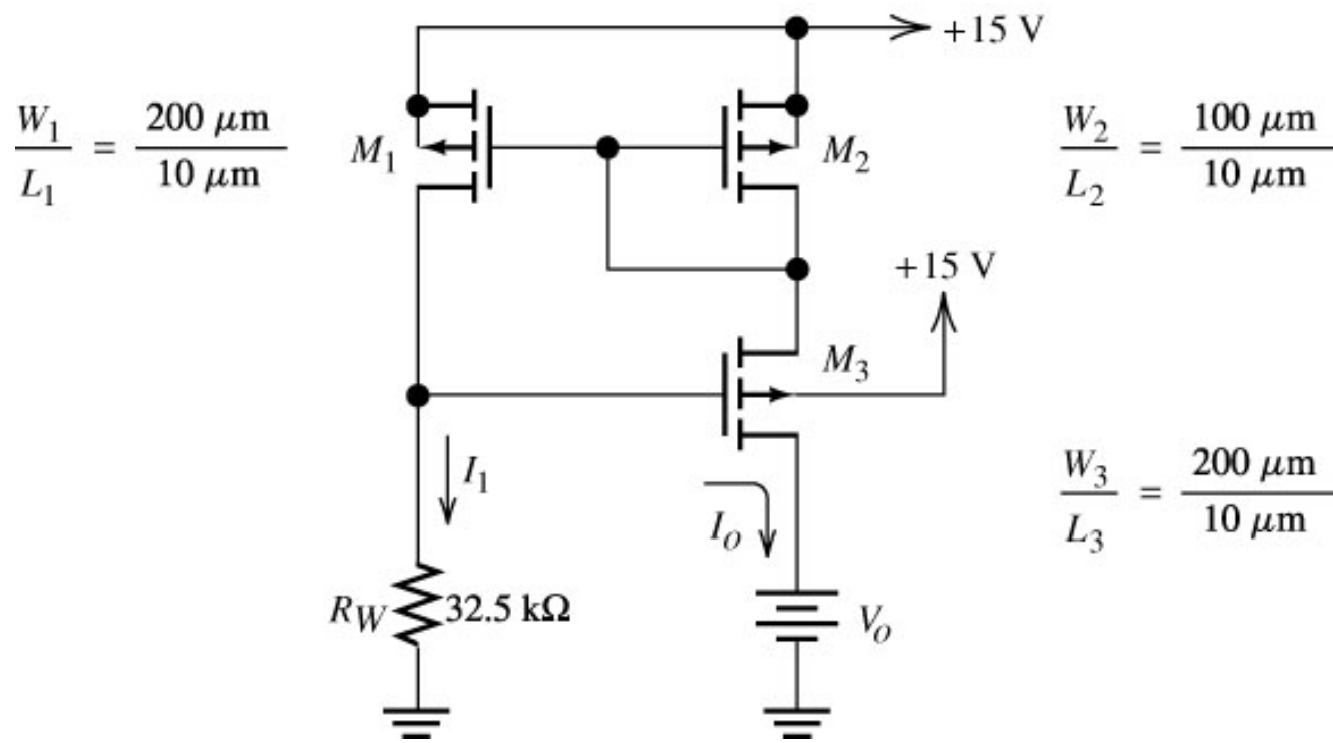

L26 - 27Apr09

Figure 7.21 One solution for Exercise 7.8.

n-channel depletion MOSFET in ohmic region

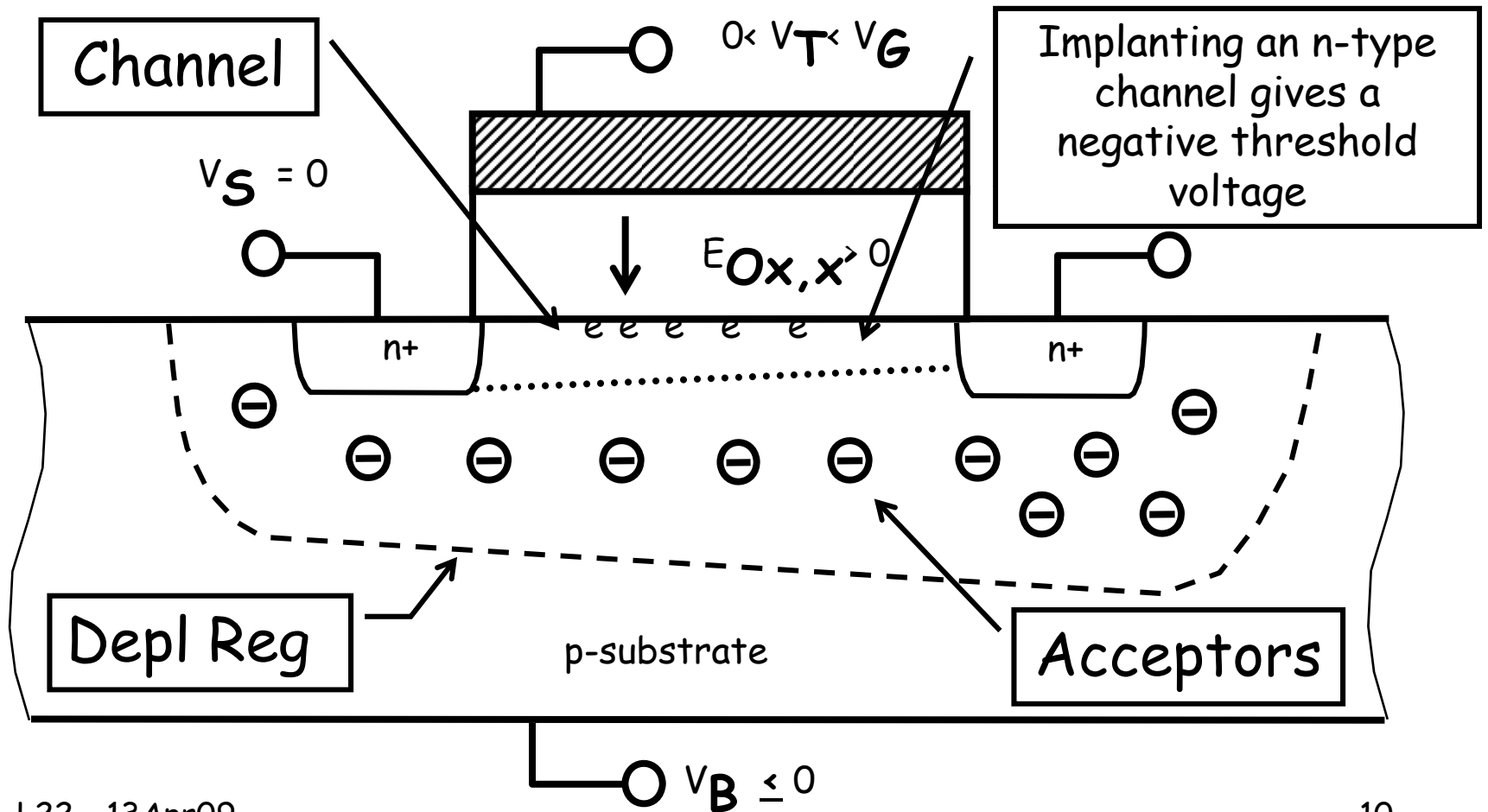

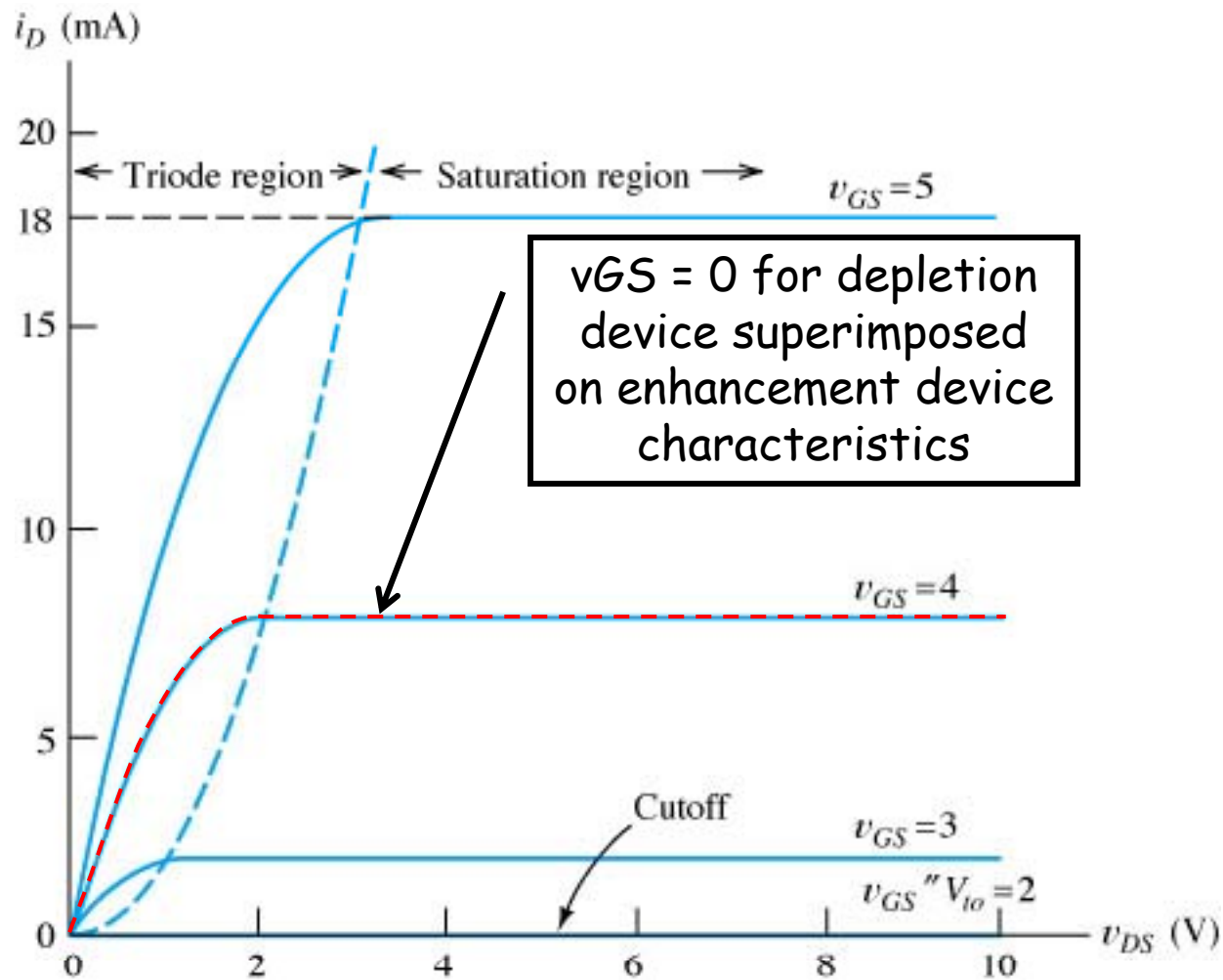


Figure 5.6 adapted to show a depletion load
Characteristic curves for an NMOS transistor.



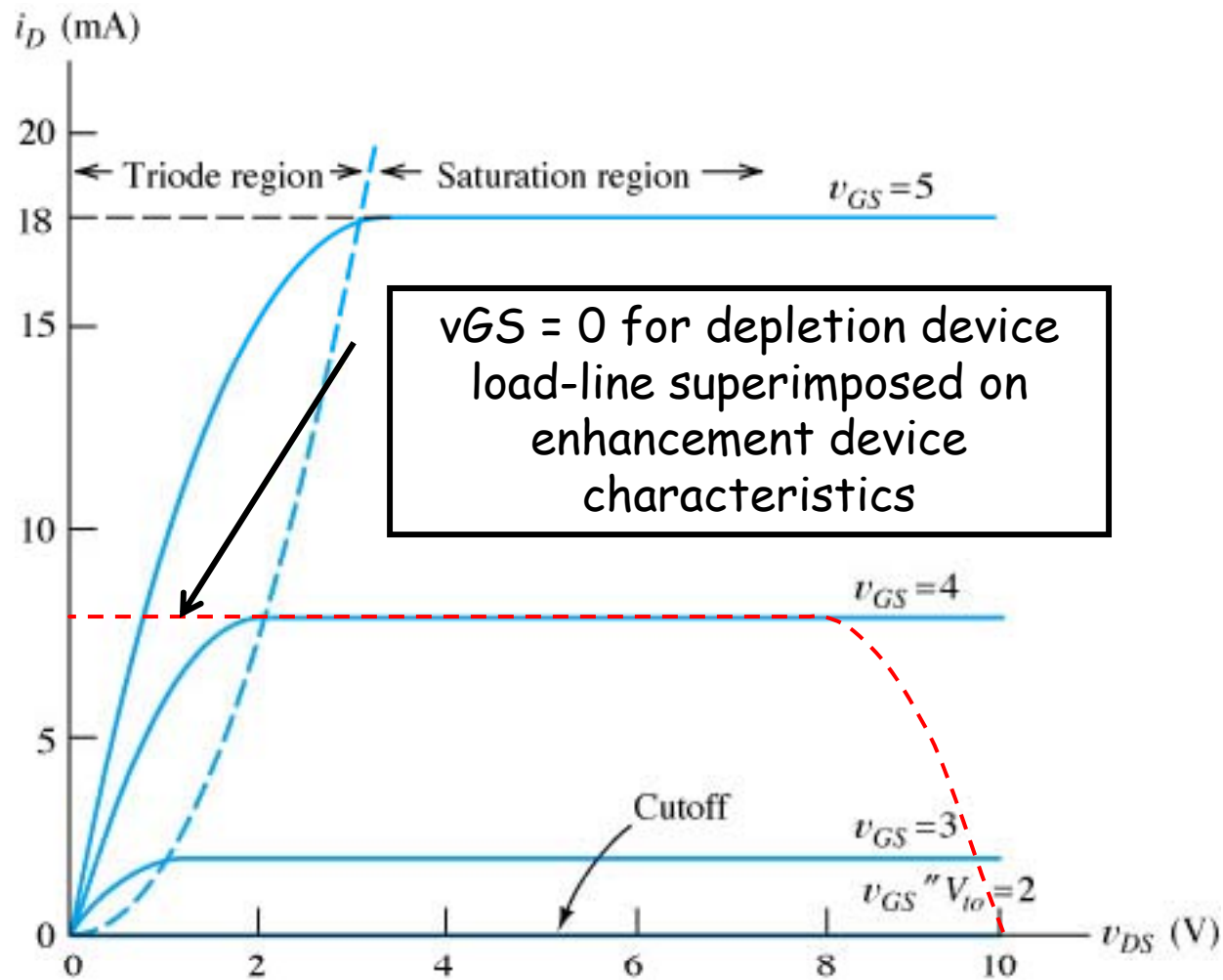


Figure 5.6 adapted to show a depletion load
Characteristic curves for an NMOS transistor.

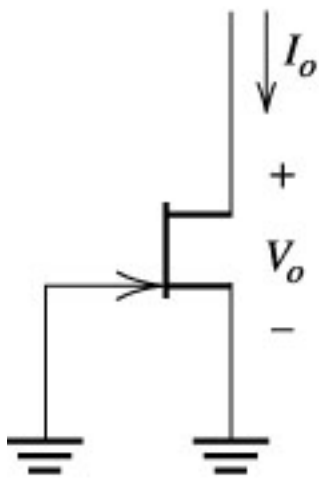

(a)

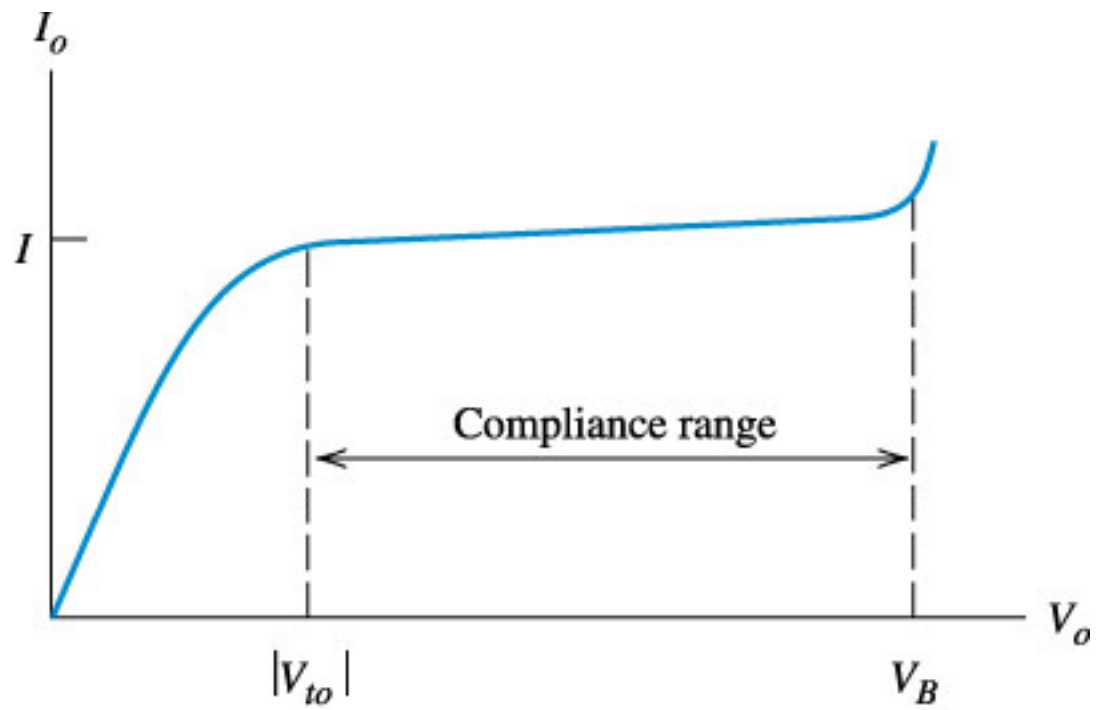

(b)

References and Endnotes

- Where not otherwise noted, figures with a figure number (e.g., Fig 3.2) are taken from:
 - Electronics, 2nd edition, by Allan R. Hambley, Prentice Hall, Upper Saddle River, NJ, © 2000.